

Name – Tapas Mazumdar

ID – 2018A8B40427P

Analog Electronics Lab #2 – Common Collector Amplifier, Darlington pair, Bootstrap configuration

Objectives

Design the provided circuit on LT Spice and calculate the following parameters

1. Voltage gain
2. Input Resistance
3. Output Resistance
4. Input voltage and current
5. Output voltage and current
6. Show input and output waveform




for the following three configurations:

- a) Common collector,
- b) Darlington pair,
- c) Bootstrap configuration.

at an operating point $V_{ce} = V_{cc}/2$. Also, record observations and write conclusions for each amplifier configuration.

Common Collector

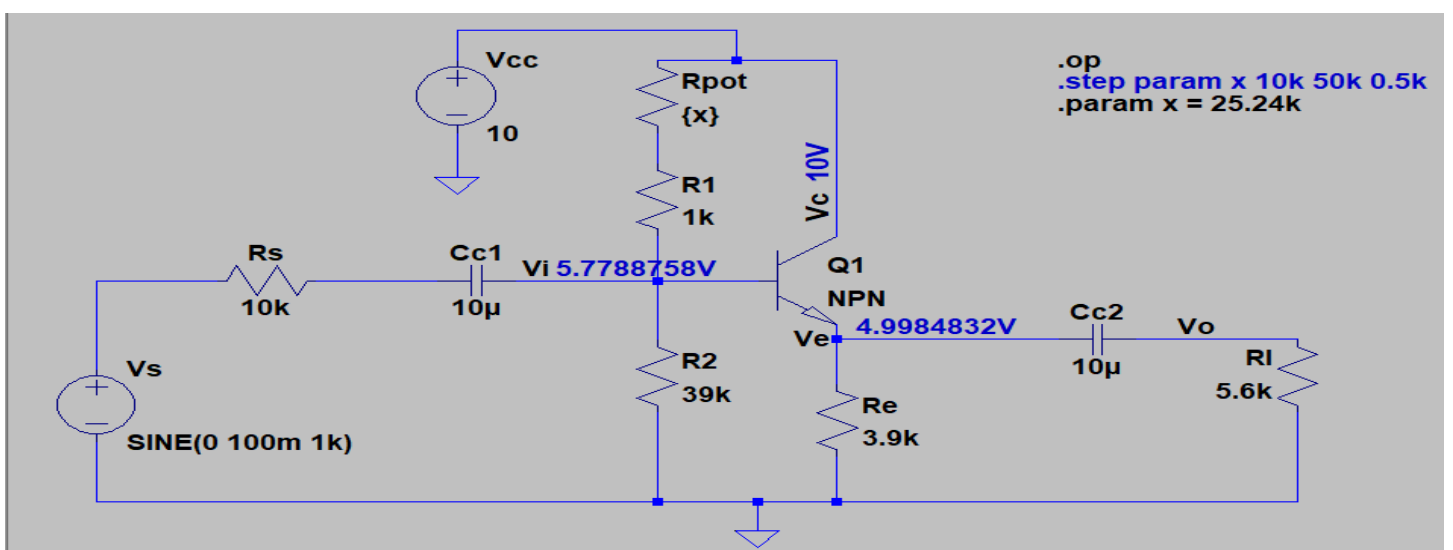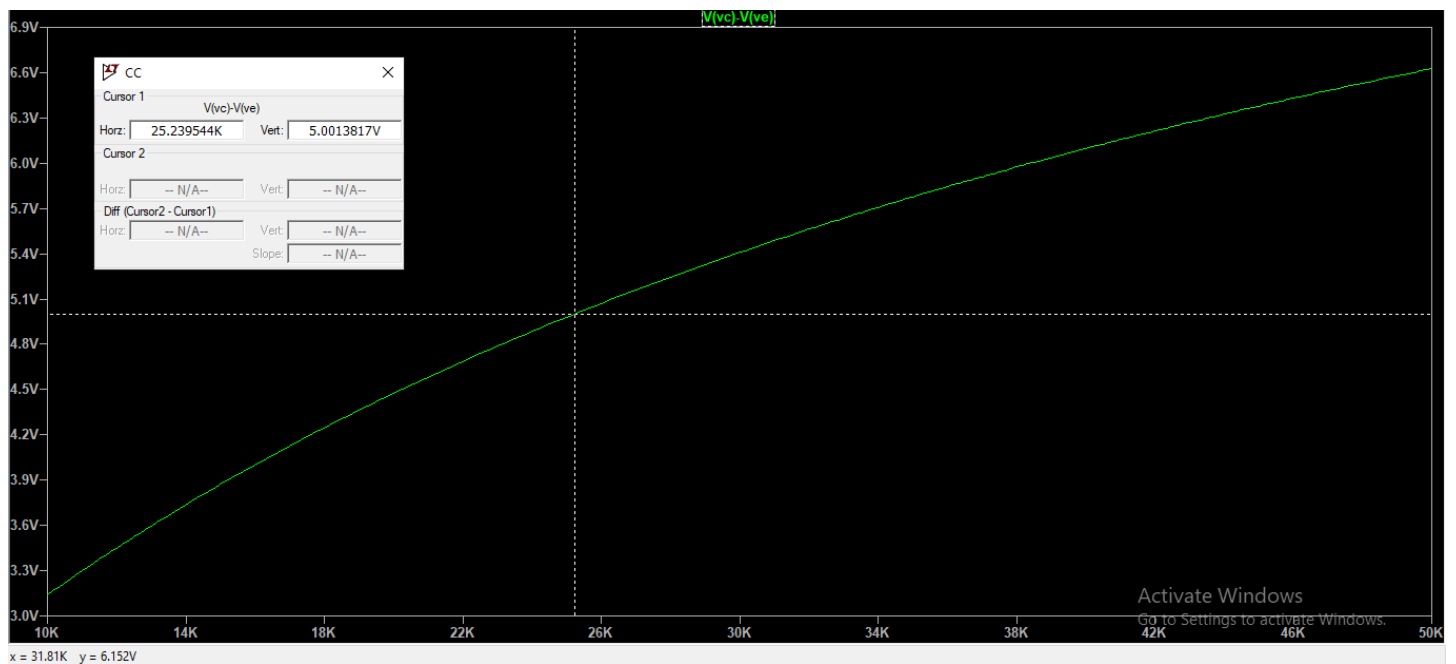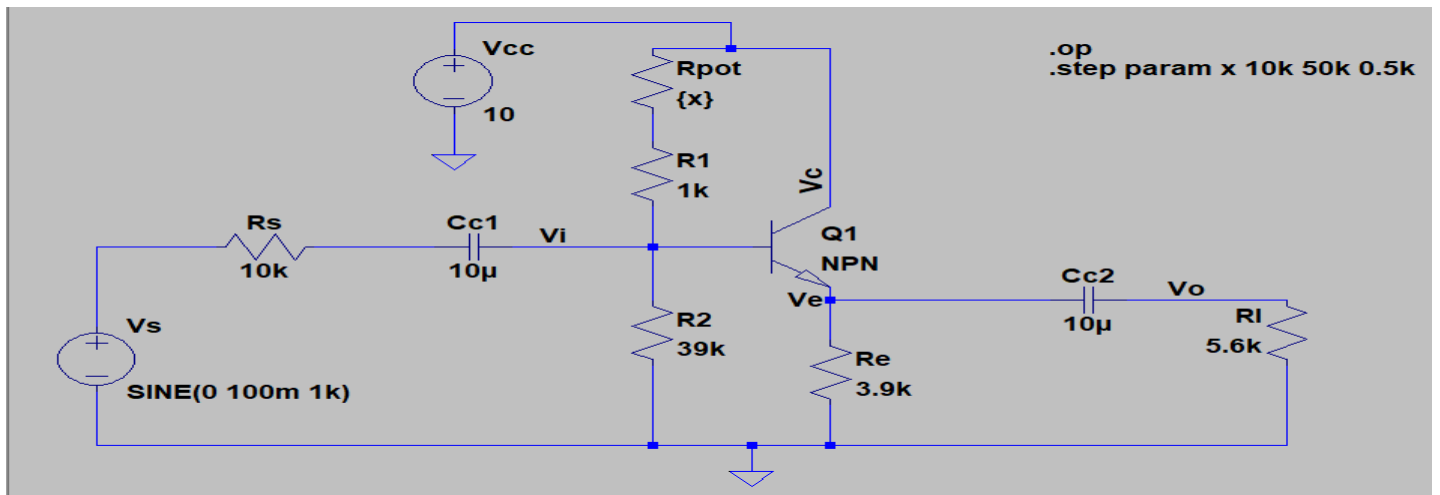Finding the value of potentiometer resistance




DC analysis using .op gives $R_{pot} = 25.24 \text{ k}\Omega$ (total = $26.24 \text{ k}\Omega$) for $V_{ce} = 5\text{V}$.

AC analysis to find voltage gain, I_{in}, I_{out}, V_{in}, V_{out} at f = 1kHz (.ac lin 1 1k 1k)

$$\text{Gain} = V(v_o)/V(v_i) = 0.0589986/0.0595167 = 0.9913 = -0.076 \text{ dB}$$

$$\text{Gain (Ai)} = I_e(Q1)/I_b(Q1) = 25.6633\mu\text{A}/0.254092\mu\text{A} = 101 = 40.1 \text{ dB}$$

 * D:\BITS\BITS SEM 6\INSTR F341 (AnE)\Lab2\CC\CC.asc



--- AC Analysis ---

frequency:	1000	Hz		
V(vc) :	mag:	0	phase:	0°
V(vi) :	mag:	0.0595167	phase:	0.0352325°
V(ve) :	mag:	0.0589988	phase:	0.0346508°
V(n001) :	mag:	0.0572485	phase:	0.0352325°
V(vo) :	mag:	0.0589986	phase:	0.197488°
V(n003) :	mag:	0.0595167	phase:	-0.0267943°
V(n002) :	mag:	0.1	phase:	0°
Ic(Q1) :	mag:	2.54092e-005	phase:	0.1015°
Ib(Q1) :	mag:	2.54092e-007	phase:	0.1015°
Ie(Q1) :	mag:	2.56633e-005	phase:	-179.899°
I(Cc1) :	mag:	4.04833e-006	phase:	-179.961°
I(Cc2) :	mag:	1.05355e-005	phase:	-179.803°
I(Rs) :	mag:	4.04833e-006	phase:	-179.961°
I(Rl) :	mag:	1.05355e-005	phase:	-179.803°
I(Re) :	mag:	1.51279e-005	phase:	0.0346508°
I(R2) :	mag:	1.52607e-006	phase:	0.0352325°
I(Rpot) :	mag:	2.26817e-006	phase:	-179.965°
I(R1) :	mag:	2.26817e-006	phase:	-179.965°
I(Vcc) :	mag:	2.31411e-005	phase:	-179.892°
I(Vs) :	mag:	4.04833e-006	phase:	-179.961°

Other parameters:


$$V_{in} = 0.0595167 \text{ V} \angle 0.0352325^\circ$$

$$I_{in} = 4.04833 \mu\text{A} \angle -179.961^\circ$$

$$V_{out} = 0.0589986 \text{ V} \angle 0.197488^\circ$$

$$I_{out} = 10.5355 \mu\text{A} \angle -179.803^\circ$$

Input and Output waveforms (.tran 10m)

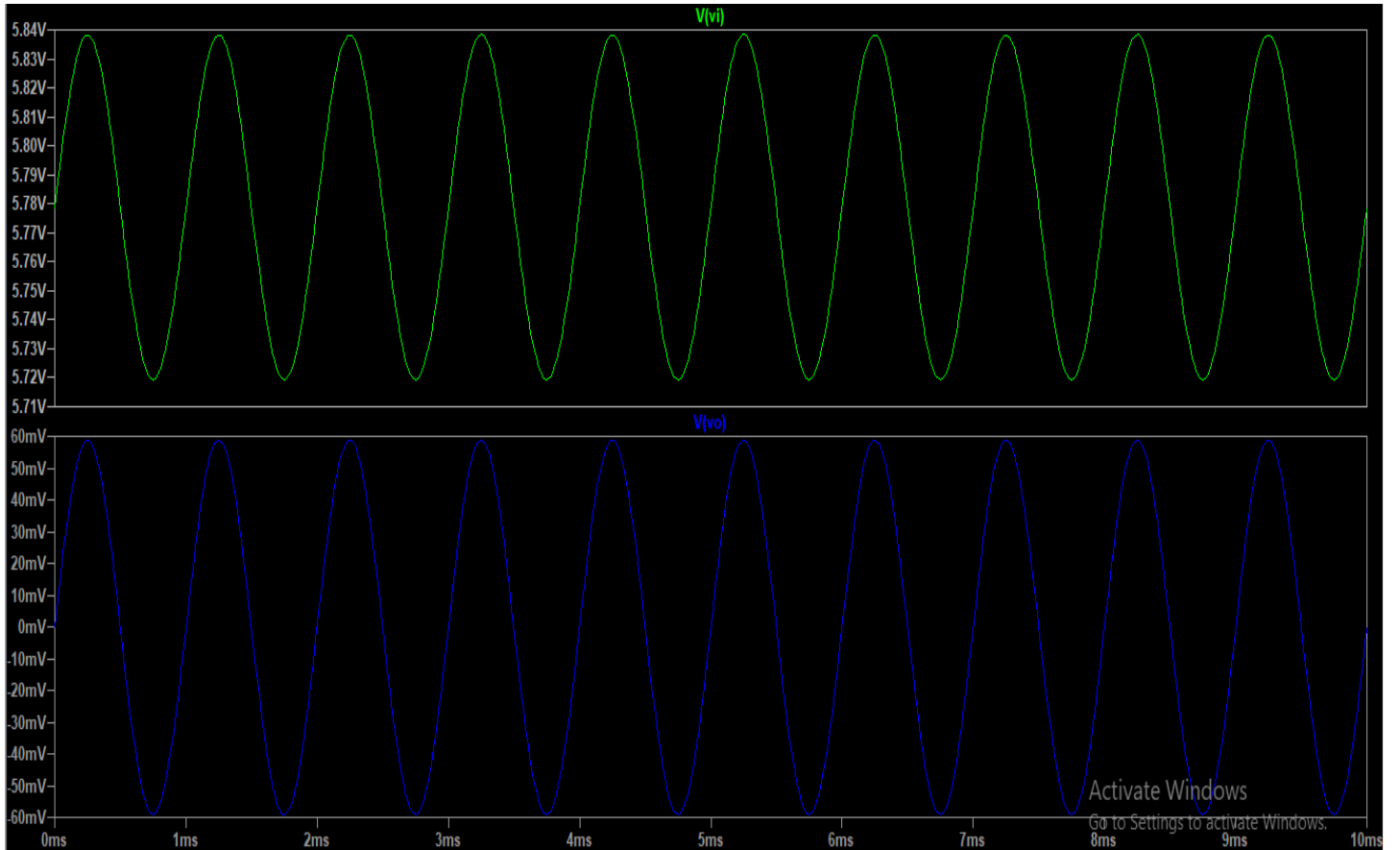

Input resistance (R_{in})

DC input resistance: infinite (as input capacitor blocks all dc voltage)

AC input resistance:


* D:\BITS\BITS SEM 6\INSTR F341 (AnE)\Lab2\CC\CC.asc					×
--- AC Analysis ---					
frequency:	1000	Hz			
V(vc):	mag:	0	phase:	0°	voltage
V(vi):	mag:	0.0595167	phase:	0.0352325°	voltage
V(ve):	mag:	0.0589988	phase:	0.0346508°	voltage
V(n001):	mag:	0.0572485	phase:	0.0352325°	voltage
V(vo):	mag:	0.0589986	phase:	0.197488°	voltage
V(n003):	mag:	0.0595167	phase:	-0.0267943°	voltage
V(n002):	mag:	0.1	phase:	0°	voltage
Ic(Q1):	mag:	2.54092e-005	phase:	0.1015°	device_current
Ib(Q1):	mag:	2.54092e-007	phase:	0.1015°	device_current
Ie(Q1):	mag:	2.56633e-005	phase:	-179.899°	device_current
I(Cc1):	mag:	4.04833e-006	phase:	-179.961°	device_current
I(Cc2):	mag:	1.05355e-005	phase:	-179.803°	device_current
I(Rs):	mag:	4.04833e-006	phase:	-179.961°	device_current
I(Rl):	mag:	1.05355e-005	phase:	-179.803°	device_current
I(Re):	mag:	1.51279e-005	phase:	0.0346508°	device_current
I(R2):	mag:	1.52607e-006	phase:	0.0352325°	device_current
I(Rpot):	mag:	2.26817e-006	phase:	-179.965°	device_current
I(R1):	mag:	2.26817e-006	phase:	-179.965°	device_current
I(Vcc):	mag:	2.31411e-005	phase:	-179.892°	device_current
I(Vs):	mag:	4.04833e-006	phase:	-179.961°	device_current

$$R_{in} = \frac{V_{in}}{I_{in}} = \frac{V(vi)}{I(Vs)} = \frac{0.0595167}{4.04833 \times 10^{-6}} = 14.7 \text{ k}\Omega$$

Output resistance (R_{out})

DC output resistance: 5.6 k Ω

AC output resistance:



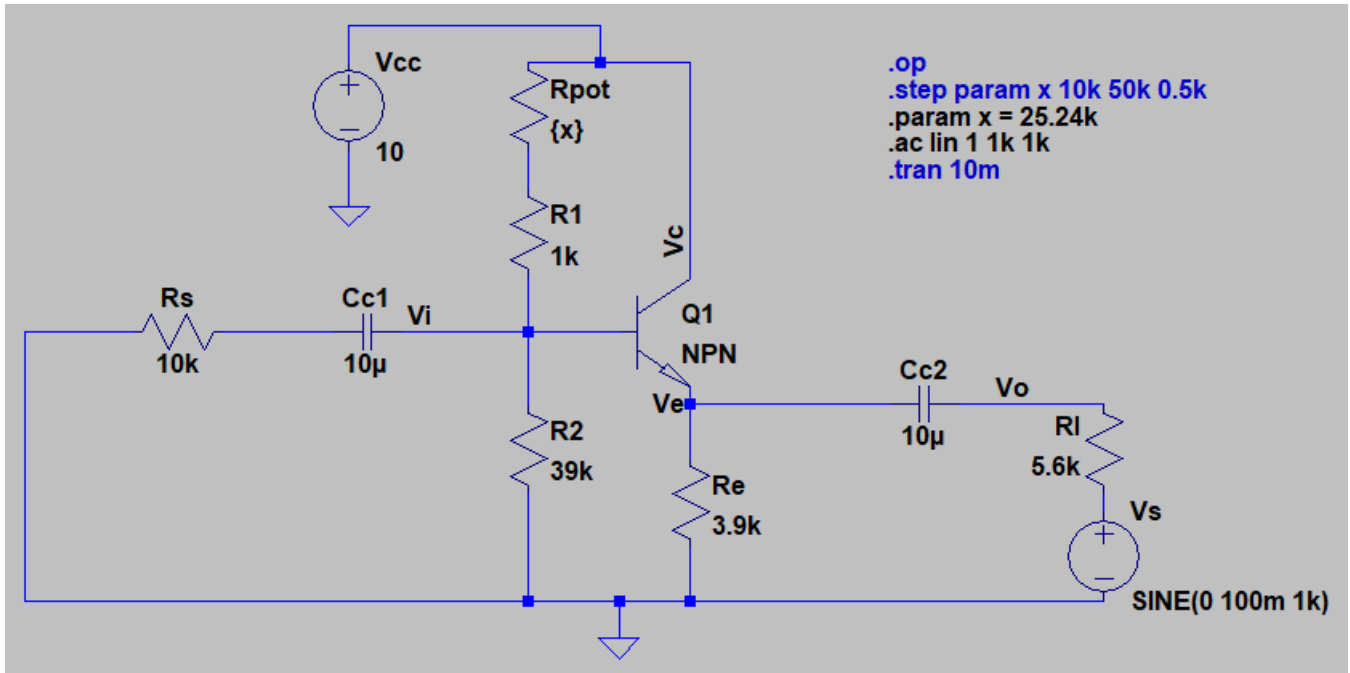


* D:\BITS\BITS SEM 6\INSTR F341 (AnE)\Lab2\CC\CC.asc					
--- AC Analysis ---					
frequency:	1000	Hz			
V(vc):	mag: 0	phase: 0°		voltage	
V(vi):	mag: 0.00104312	phase: 0.106299°		voltage	
V(ve):	mag: 0.00139127	phase: 0.120234°		voltage	
V(n001):	mag: 0.00100336	phase: 0.106299°		voltage	
V(n003):	mag: 0.1	phase: 0°		voltage	
V(vo):	mag: 0.00141941	phase: -11.2671°		voltage	
V(n002):	mag: 0.00104311	phase: 0.197488°		voltage	
Ic(Q1):	mag: 1.70811e-005	phase: -179.838°		device_current	
Ib(Q1):	mag: 1.70811e-007	phase: -179.838°		device_current	
Ie(Q1):	mag: 1.72519e-005	phase: 0.161987°		device_current	
I(Cc1):	mag: 1.04311e-007	phase: 0.197488°		device_current	
I(Cc2):	mag: 1.76086e-005	phase: 0.161141°		device_current	
I(Rs):	mag: 1.04311e-007	phase: 0.197488°		device_current	
I(Rl):	mag: 1.76086e-005	phase: 0.161141°		device_current	
I(Re):	mag: 3.56736e-007	phase: 0.120234°		device_current	
I(R2):	mag: 2.67466e-008	phase: 0.106299°		device_current	
I(Rpot):	mag: 3.97529e-008	phase: -179.894°		device_current	
I(R1):	mag: 3.97529e-008	phase: -179.894°		device_current	
I(Vcc):	mag: 1.71208e-005	phase: 0.161857°		device_current	
I(Vs):	mag: 1.76086e-005	phase: -179.839°		device_current	

$$R_{out} = \frac{V_{out}}{I_{out}} = \frac{V(vo)}{I(Vs)} = \frac{0.00141941}{1.76086 \times 10^{-5}} = 80.61 \Omega$$

Darlington Pair

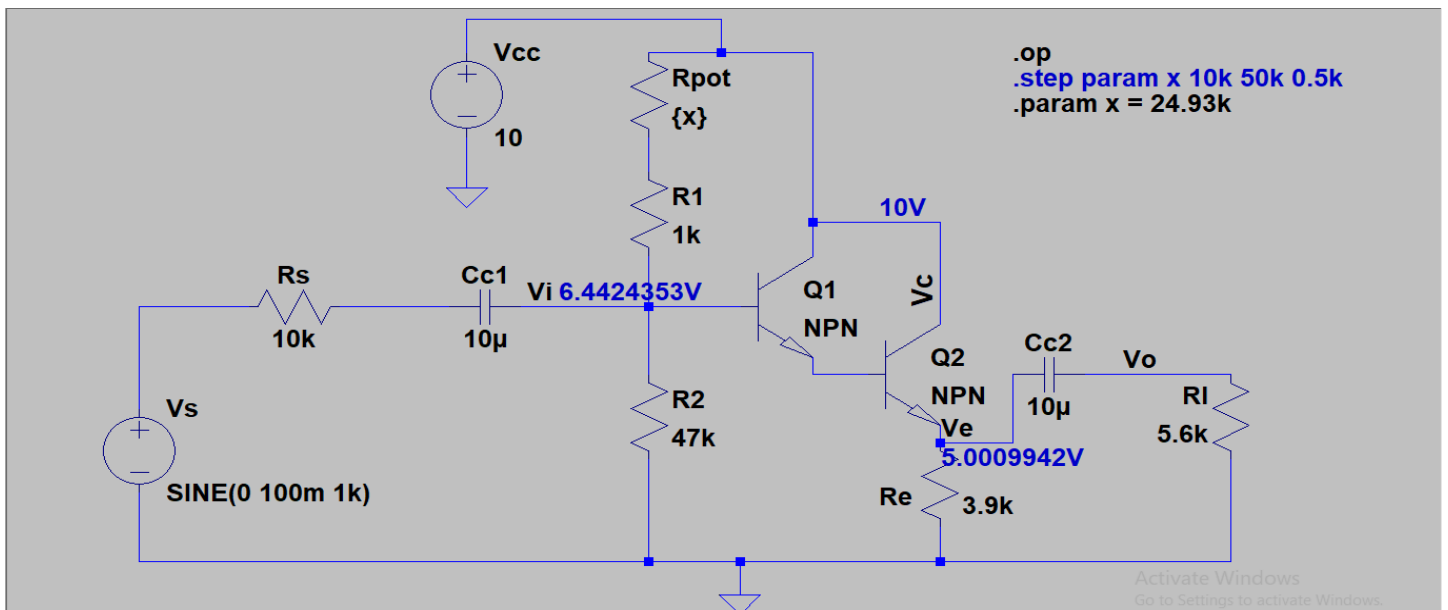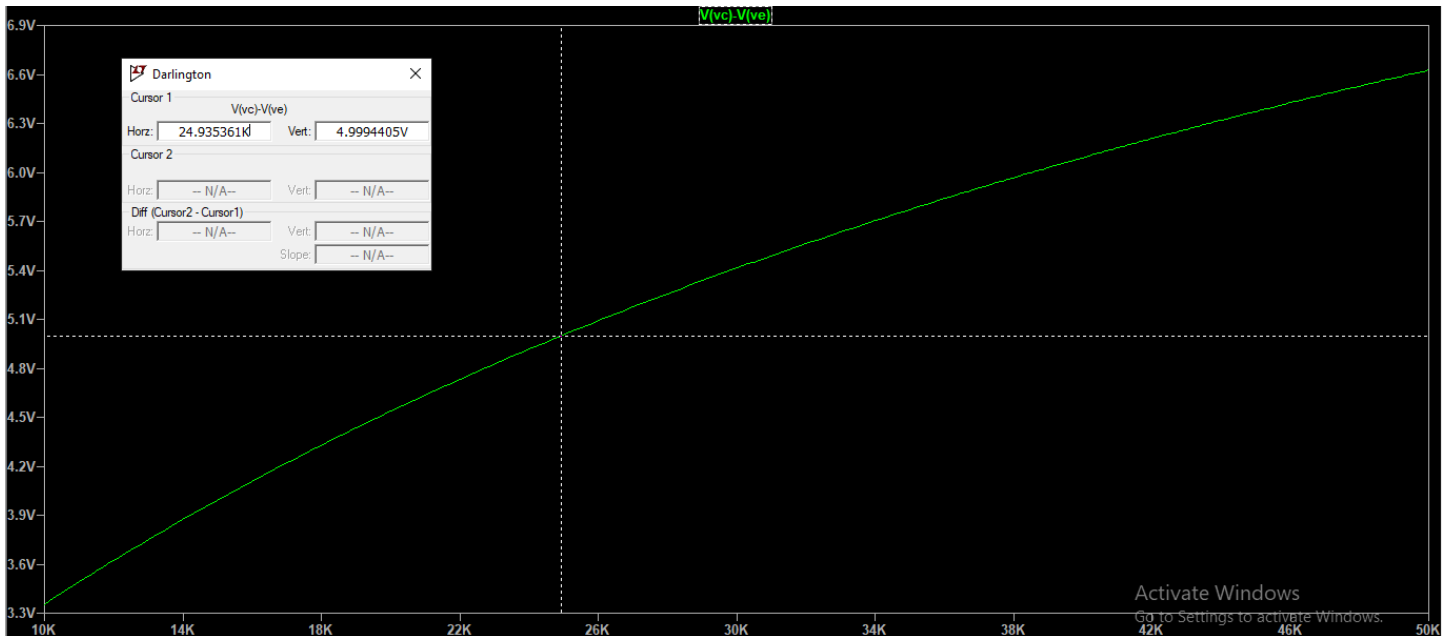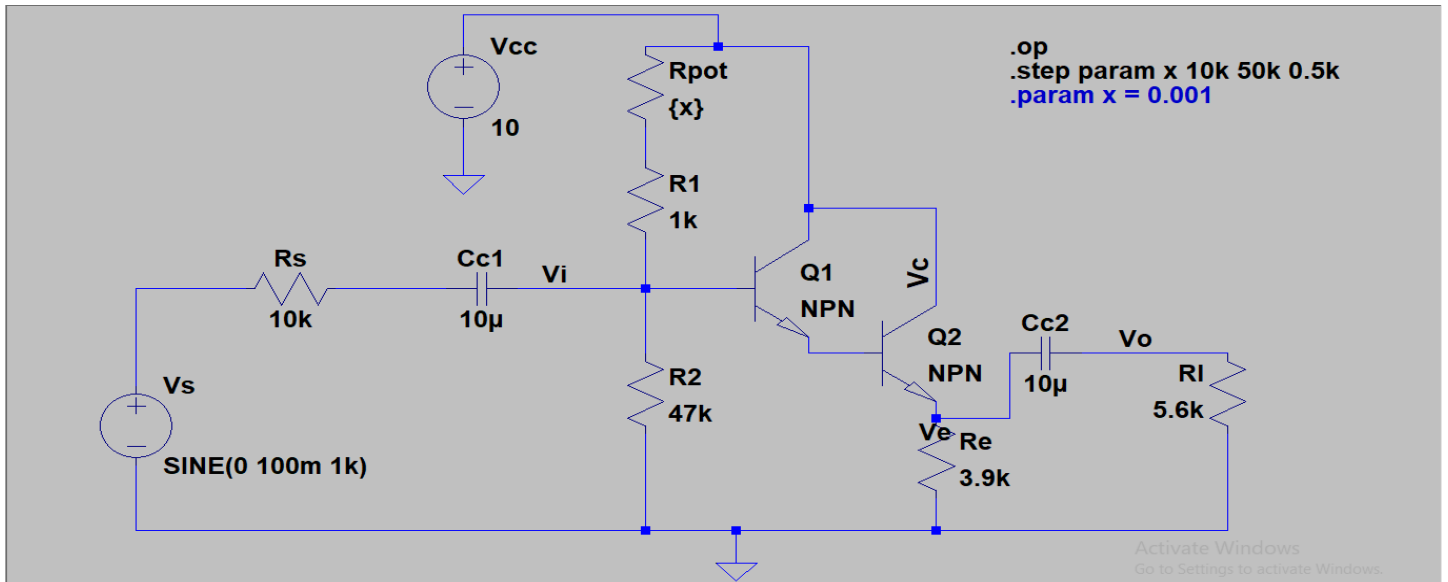Finding the value of potentiometer resistance




DC analysis using .op gives $R_{pot} = 24.93 \text{ k}\Omega$ (total = $25.93 \text{ k}\Omega$) for $V_{ce} = 5\text{V}$.

AC analysis to find voltage gain, I_{in} , I_{out} , V_{in} , V_{out} at $f = 1\text{kHz}$ (.ac lin 1 1k 1k)

$$\text{Gain (Av)} = V(v_o)/V(v_i) = 0.0614665/0.0625454 = 0.983 = -0.151 \text{ dB}$$

$$\text{Gain (Ai)} = I_e(Q2)/I_b(Q1) = 26.7369\mu\text{A}/2.62107\text{nA} = 10200.76 = 80.17 \text{ dB}$$

 * D:\BITS\BITS SEM 6\INSTR F341 (AnE)\Lab2\Darlington\Darlington.asc

×

--- AC Analysis ---

frequency:	1000	Hz		
V(vc) :	mag:	0	phase:	0°
V(vi) :	mag:	0.0625454	phase:	0.0341373°
V(n004) :	mag:	0.0620061	phase:	0.0335659°
V(n001) :	mag:	0.0601333	phase:	0.0341373°
V(ve) :	mag:	0.0614668	phase:	0.0329845°
V(vo) :	mag:	0.0614665	phase:	0.195822°
V(n003) :	mag:	0.0625454	phase:	-0.0204702°
V(n002) :	mag:	0.1	phase:	0°
Ic(Q2) :	mag:	2.64721e-005	phase:	0.0998332°
Ib(Q2) :	mag:	2.64721e-007	phase:	0.0998332°
Ie(Q2) :	mag:	2.67369e-005	phase:	-179.9°
Ic(Q1) :	mag:	2.621e-007	phase:	0.0998332°
Ib(Q1) :	mag:	2.62107e-009	phase:	0.0998317°
Ie(Q1) :	mag:	2.64721e-007	phase:	-179.9°
I(Cc1) :	mag:	3.74546e-006	phase:	-179.966°
I(Cc2) :	mag:	1.09762e-005	phase:	-179.804°
I(Rs) :	mag:	3.74546e-006	phase:	-179.966°
I(Rl) :	mag:	1.09762e-005	phase:	-179.804°
I(Re) :	mag:	1.57607e-005	phase:	0.0329845°
I(R2) :	mag:	1.33075e-006	phase:	0.0341373°
I(Rpot) :	mag:	2.41209e-006	phase:	-179.966°
I(R1) :	mag:	2.41209e-006	phase:	-179.966°
I(Vcc) :	mag:	2.43222e-005	phase:	-179.894°
I(Vs) :	mag:	3.74546e-006	phase:	-179.966°

Other parameters:


$$V_{in} = 0.0625454 \text{ V} \angle 0.0341373^\circ$$

$$I_{in} = 3.74546 \mu\text{A} \angle -179.966^\circ$$

$$V_{out} = 0.0614665 \text{ V} \angle 0.195822^\circ$$

$$I_{out} = 10.9762 \mu\text{A} \angle -179.804^\circ$$


Input and Output waveforms (.tran 10m)

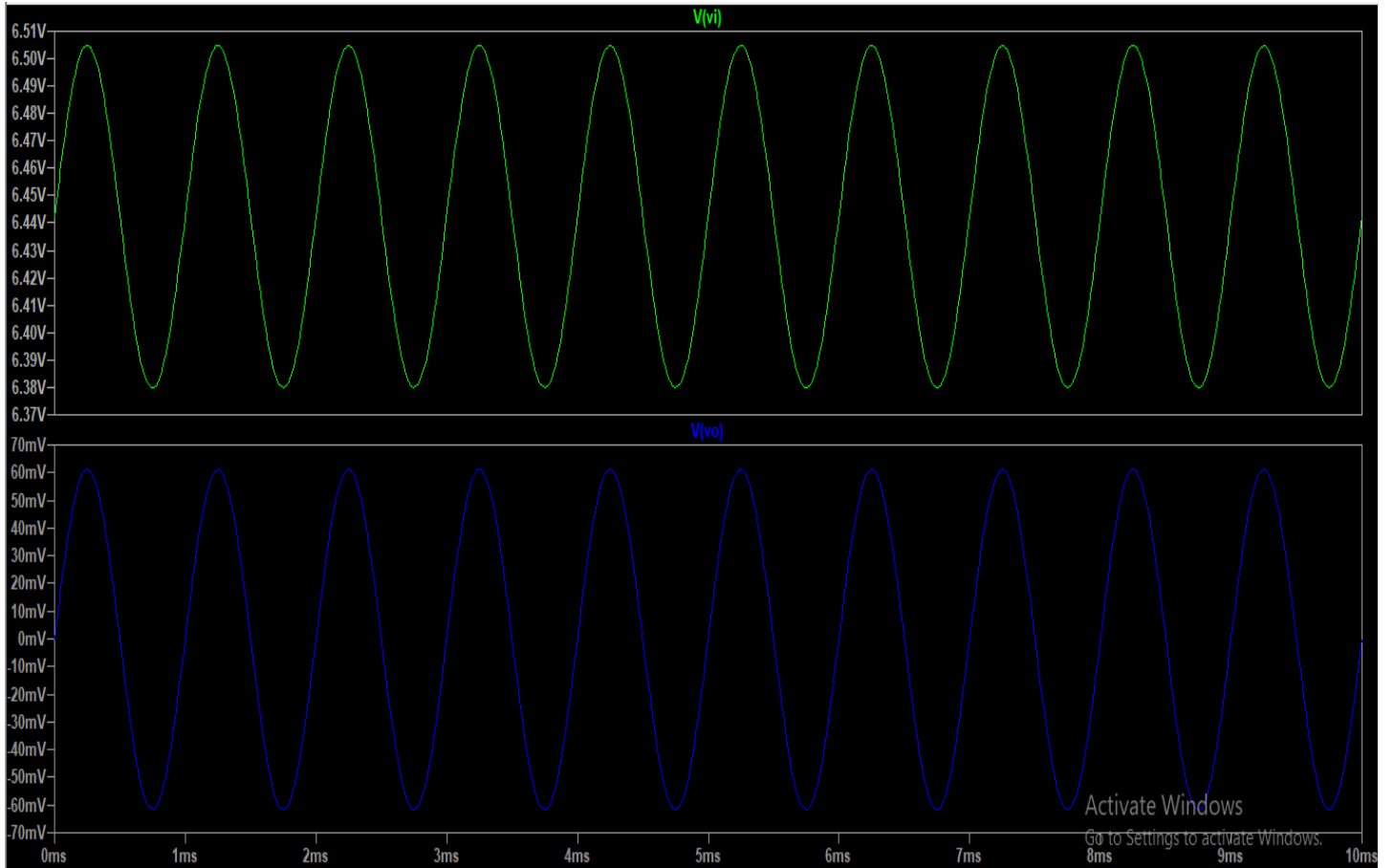

Input resistance (R_{in})

DC input resistance: infinite (as input capacitor blocks all dc voltage)

AC input resistance:

 * D:\BITS\BITS SEM 6\INSTR F341 (AnE)\Lab2\Darlington\Darlington.asc

×

--- AC Analysis ---


frequency:	1000	Hz		
V(vc) :	mag:	0	phase:	0°
V(vi) :	mag:	0.0625454	phase:	0.0341373°
V(n004) :	mag:	0.0620061	phase:	0.0335659°
V(n001) :	mag:	0.0601333	phase:	0.0341373°
V(ve) :	mag:	0.0614668	phase:	0.0329845°
V(vo) :	mag:	0.0614665	phase:	0.195822°
V(n003) :	mag:	0.0625454	phase:	-0.0204702°
V(n002) :	mag:	0.1	phase:	0°
Ic(Q2) :	mag:	2.64721e-005	phase:	0.0998332°
Ib(Q2) :	mag:	2.64721e-007	phase:	0.0998332°
Ie(Q2) :	mag:	2.67369e-005	phase:	-179.9°
Ic(Q1) :	mag:	2.621e-007	phase:	0.0998332°
Ib(Q1) :	mag:	2.62107e-009	phase:	0.0998317°
Ie(Q1) :	mag:	2.64721e-007	phase:	-179.9°
I(Cc1) :	mag:	3.74546e-006	phase:	-179.966°
I(Cc2) :	mag:	1.09762e-005	phase:	-179.804°
I(Rs) :	mag:	3.74546e-006	phase:	-179.966°
I(Rl) :	mag:	1.09762e-005	phase:	-179.804°
I(Re) :	mag:	1.57607e-005	phase:	0.0329845°
I(R2) :	mag:	1.33075e-006	phase:	0.0341373°
I(Rpot) :	mag:	2.41209e-006	phase:	-179.966°
I(R1) :	mag:	2.41209e-006	phase:	-179.966°
I(Vcc) :	mag:	2.43222e-005	phase:	-179.894°
I(Vs) :	mag:	3.74546e-006	phase:	-179.966°

$$R_{in} = \frac{V_{in}}{I_{in}} = \frac{V(vi)}{I(Vs)} = \frac{0.0625454}{3.74546 \times 10^{-6}} = 16.7 \text{ k}\Omega$$

Output resistance (R_{out})

DC output resistance: 5.6 k Ω

AC output resistance:

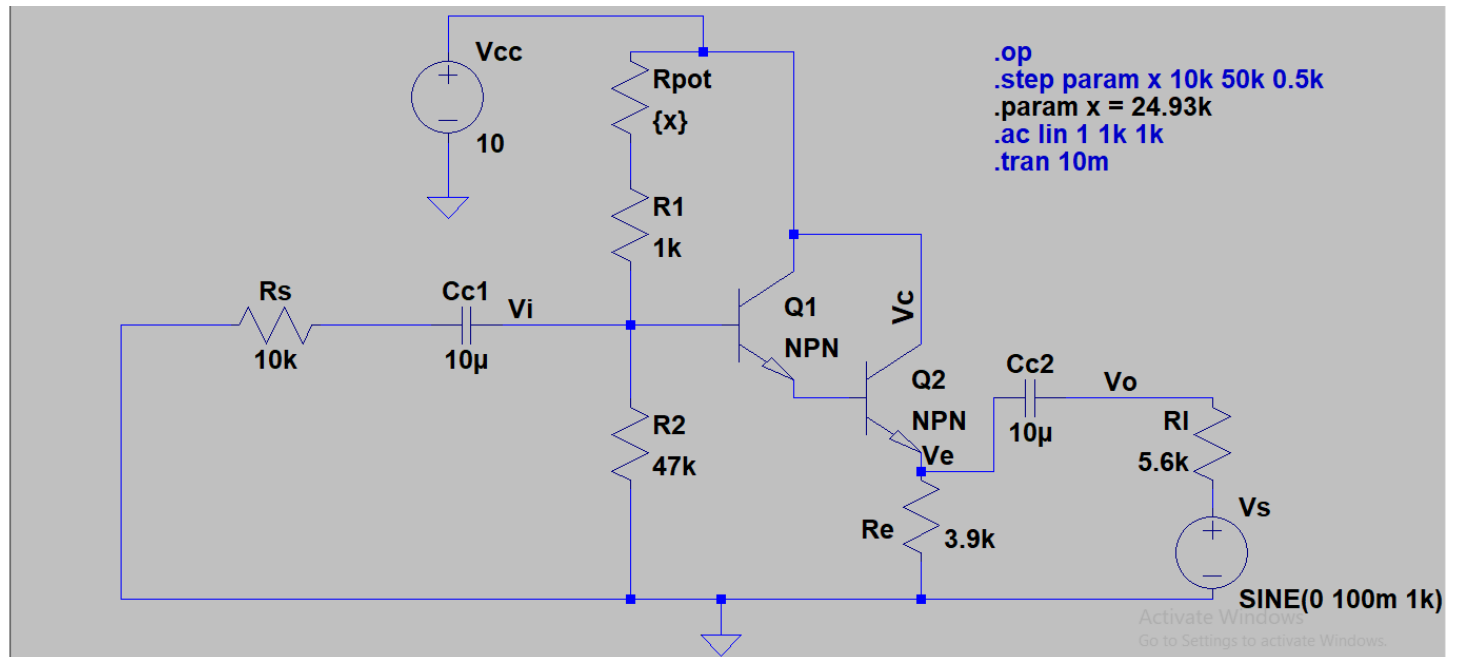

* D:\BITS\BITS SEM 6\INSTR F341 (AnE)\Lab2\Darlington\Darlington.asc

```

--- AC Analysis ---




```

frequency:	1000	Hz		
V(vc):	mag:	0	phase:	0° voltage
V(vi):	mag:	1.07599e-005	phase:	0.104633° voltage
V(n003):	mag:	0.000364645	phase:	0.159999° voltage
V(n001):	mag:	1.03449e-005	phase:	0.104633° voltage
V(ve):	mag:	0.000718529	phase:	0.160828° voltage
V(n004):	mag:	0.1	phase:	0° voltage
V(vo):	mag:	0.000771949	phase:	-21.2787° voltage
V(n002):	mag:	1.07599e-005	phase:	0.195822° voltage
Ic(Q2):	mag:	1.73708e-005	phase:	-179.838° device_current
Ib(Q2):	mag:	1.73708e-007	phase:	-179.838° device_current
Ie(Q2):	mag:	1.75445e-005	phase:	0.161682° device_current
Ic(Q1):	mag:	1.71988e-007	phase:	-179.838° device_current
Ib(Q1):	mag:	1.71988e-009	phase:	-179.838° device_current
Ie(Q1):	mag:	1.73708e-007	phase:	0.161682° device_current
I(Cc1):	mag:	1.07599e-009	phase:	0.195822° device_current
I(Cc2):	mag:	1.77288e-005	phase:	0.161673° device_current
I(Rs):	mag:	1.07599e-009	phase:	0.195822° device_current
I(Rl):	mag:	1.77288e-005	phase:	0.161673° device_current
I(Re):	mag:	1.84238e-007	phase:	0.160828° device_current
I(R2):	mag:	2.28934e-010	phase:	0.104633° device_current
I(Rpot):	mag:	4.1496e-010	phase:	-179.895° device_current
I(R1):	mag:	4.1496e-010	phase:	-179.895° device_current
I(Vcc):	mag:	1.75432e-005	phase:	0.161681° device_current
I(Vs):	mag:	1.77288e-005	phase:	-179.838° device_current

$$R_{\text{out}} = \frac{V_{\text{out}}}{I_{\text{out}}} = \frac{V(\text{vo})}{I(\text{Vs})} = \frac{0.000771949}{1.77288 \times 10^{-5}} = 43.54 \, \Omega$$

Bootstrap Configuration

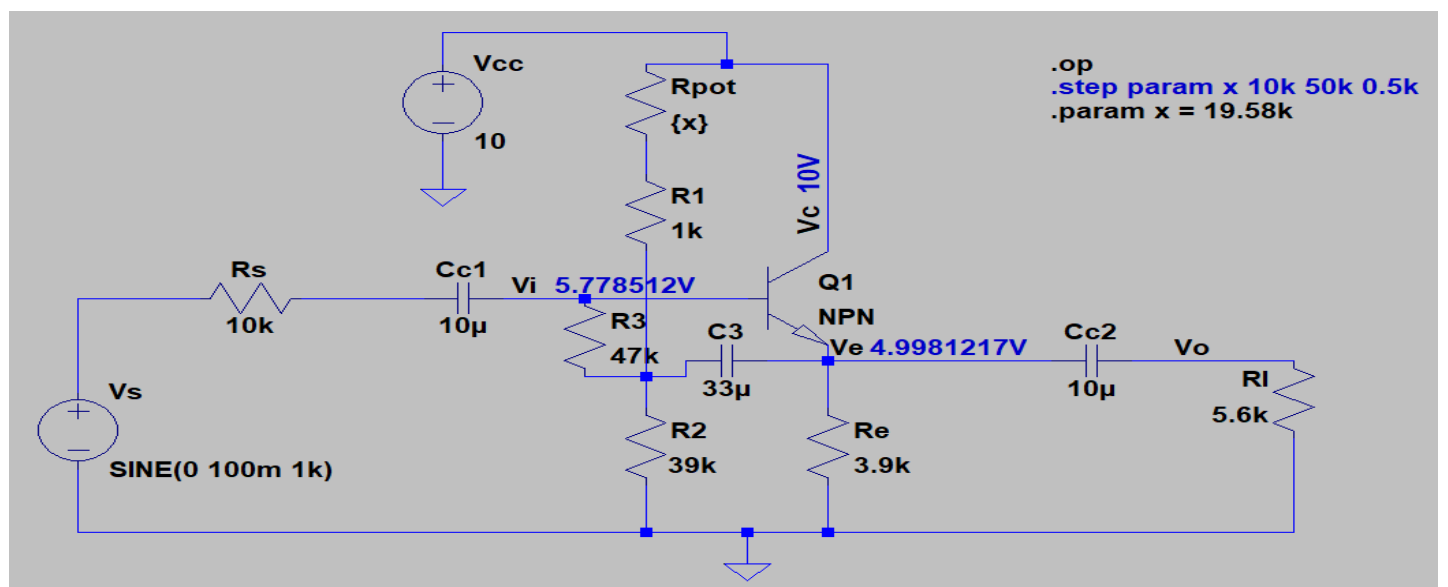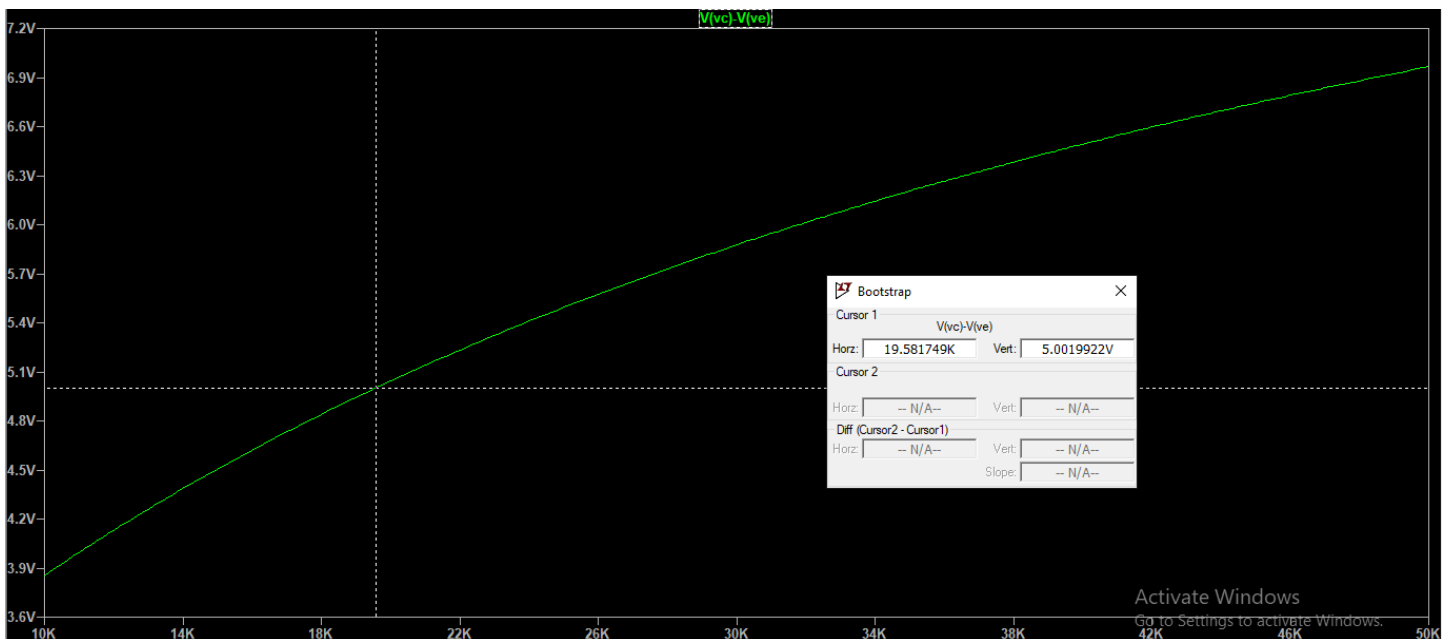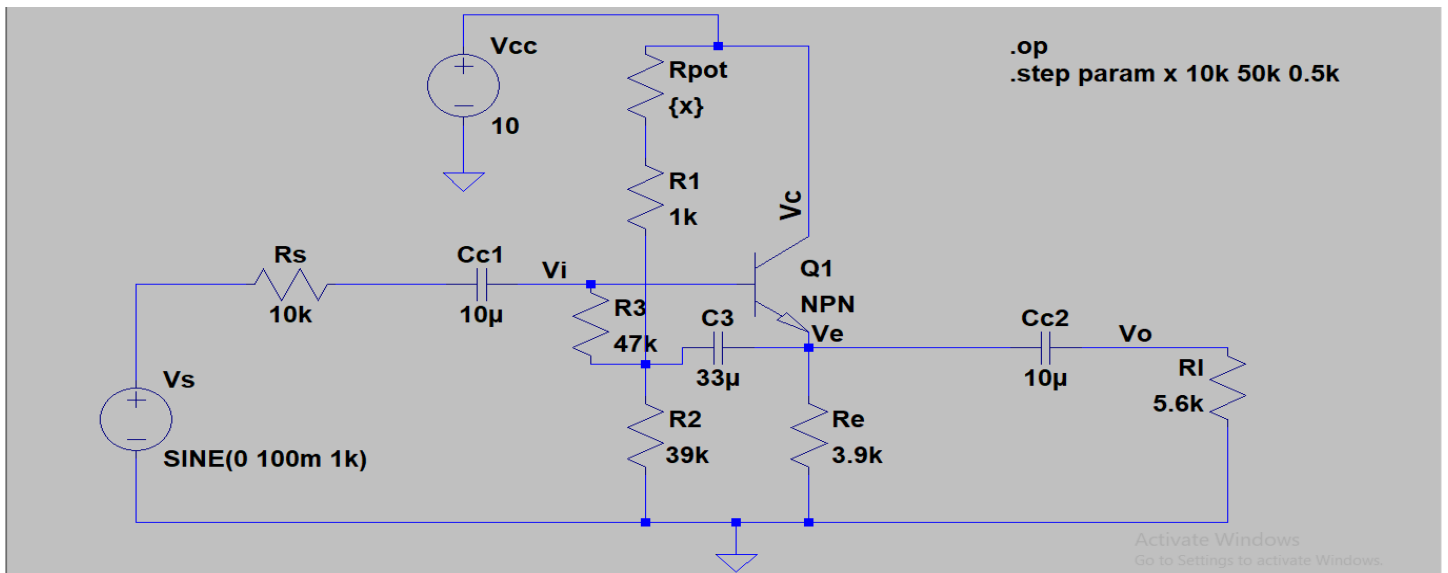Finding the value of potentiometer resistance




DC analysis using .op gives $R_{pot} = 19.58 \text{ k}\Omega$ (total = $20.58 \text{ k}\Omega$) for $V_{ce} = 5V$.

AC analysis to find voltage gain, I_{in} , I_{out} , V_{in} , V_{out} at $f = 1\text{kHz}$ (.ac lin 1 1k 1k)

$$\text{Gain} = V(v_o)/V(v_i) = 0.0940859/0.0950528 = 0.9898 = -0.089 \text{ dB}$$

$$\text{Gain (Ai)} = I_e(Q1)/I_b(Q1) = 47.8894\mu\text{A}/0.474152\mu\text{A} = 101 = 40.1 \text{ dB}$$

 * D:\BITS\BITS SEM 6\INSTR F341 (AnE)\Lab2\Bootstrap\Bootstrap.asc

×

--- AC Analysis ---

frequency:	1000	Hz		
V(vc) :	mag:	0	phase:	0°
V(vi) :	mag:	0.0950528	phase:	0.00562132°
V(ve) :	mag:	0.0940863	phase:	0.00500168°
V(n001) :	mag:	0.0895146	phase:	0.0254538°
V(n004) :	mag:	0.0940863	phase:	0.0254538°
V(vo) :	mag:	0.0940859	phase:	0.167839°
V(n003) :	mag:	0.0950528	phase:	0.000875256°
V(n002) :	mag:	0.1	phase:	0°
Ic(Q1) :	mag:	4.74152e-005	phase:	0.0659414°
Ib(Q1) :	mag:	4.74152e-007	phase:	0.0659414°
Ie(Q1) :	mag:	4.78894e-005	phase:	-179.934°
I(C3) :	mag:	6.96364e-006	phase:	0.0312136°
I(Cc1) :	mag:	4.94716e-007	phase:	179.983°
I(Cc2) :	mag:	1.68011e-005	phase:	-179.832°
I(R3) :	mag:	2.05761e-008	phase:	-1.92423°
I(Rs) :	mag:	4.94716e-007	phase:	179.983°
I(Rl) :	mag:	1.68011e-005	phase:	-179.832°
I(Re) :	mag:	2.41247e-005	phase:	0.00500168°
I(R2) :	mag:	2.41247e-006	phase:	0.0254538°
I(Rpot) :	mag:	4.57174e-006	phase:	-179.975°
I(R1) :	mag:	4.57174e-006	phase:	-179.975°
I(Vcc) :	mag:	4.28435e-005	phase:	-179.93°
I(Vs) :	mag:	4.94716e-007	phase:	179.983°

Other parameters:


$$V_{in} = 0.0950528 \text{ V} \angle 0.00562132^\circ$$

$$I_{in} = 0.494716 \mu\text{A} \angle 179.983^\circ$$

$$V_{out} = 0.0940859 \text{ V} \angle 0.167839^\circ$$

$$I_{out} = 16.8011 \mu\text{A} \angle -179.832^\circ$$

Input and Output waveforms (.tran 10m)

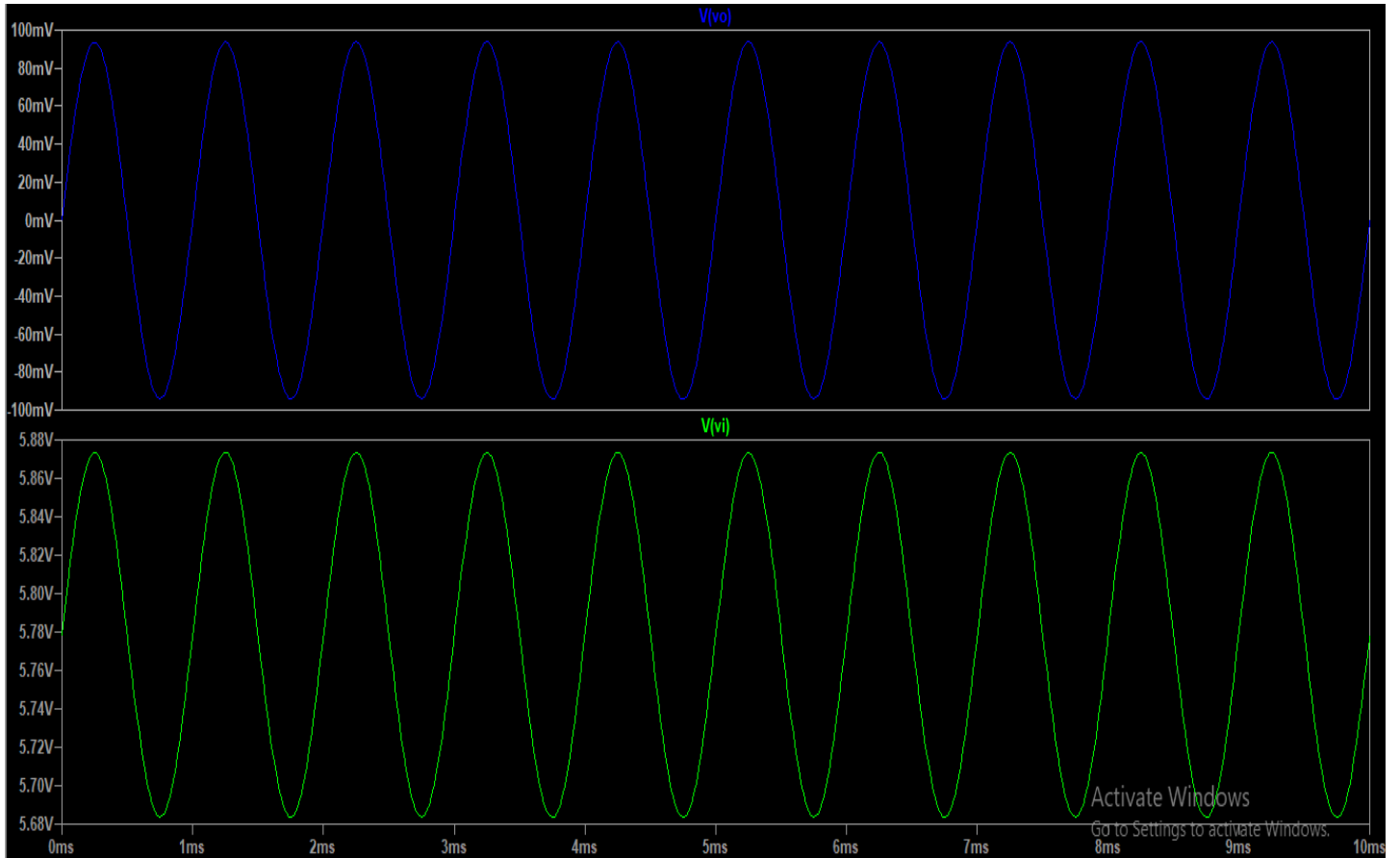

Input resistance (R_{in})

DC input resistance: infinite (as input capacitor blocks all dc voltage)

AC input resistance:

 * D:\BITS\BITS SEM 6\INSTR F341 (AnE)\Lab2\Bootstrap\Bootstrap.asc

×

--- AC Analysis ---


frequency:	1000	Hz		
V(vc) :	mag:	0	phase:	0°
V(vi) :	mag:	0.0950528	phase:	0.00562132°
V(ve) :	mag:	0.0940863	phase:	0.00500168°
V(n001) :	mag:	0.0895146	phase:	0.0254538°
V(n004) :	mag:	0.0940863	phase:	0.0254538°
V(vo) :	mag:	0.0940859	phase:	0.167839°
V(n003) :	mag:	0.0950528	phase:	0.000875256°
V(n002) :	mag:	0.1	phase:	0°
Ic(Q1) :	mag:	4.74152e-005	phase:	0.0659414°
Ib(Q1) :	mag:	4.74152e-007	phase:	0.0659414°
Ie(Q1) :	mag:	4.78894e-005	phase:	-179.934°
I(C3) :	mag:	6.96364e-006	phase:	0.0312136°
I(Cc1) :	mag:	4.94716e-007	phase:	179.983°
I(Cc2) :	mag:	1.68011e-005	phase:	-179.832°
I(R3) :	mag:	2.05761e-008	phase:	-1.92423°
I(Rs) :	mag:	4.94716e-007	phase:	179.983°
I(Rl) :	mag:	1.68011e-005	phase:	-179.832°
I(Re) :	mag:	2.41247e-005	phase:	0.00500168°
I(R2) :	mag:	2.41247e-006	phase:	0.0254538°
I(Rpot) :	mag:	4.57174e-006	phase:	-179.975°
I(R1) :	mag:	4.57174e-006	phase:	-179.975°
I(Vcc) :	mag:	4.28435e-005	phase:	-179.93°
I(Vs) :	mag:	4.94716e-007	phase:	179.983°

$$R_{in} = \frac{V_{in}}{I_{in}} = \frac{V(vi)}{I(Vs)} = \frac{0.0950528}{4.94716 \times 10^{-7}} = 192.136 \text{ k}\Omega$$

Output resistance (R_{out})

DC output resistance: 5.6 k Ω

AC output resistance:

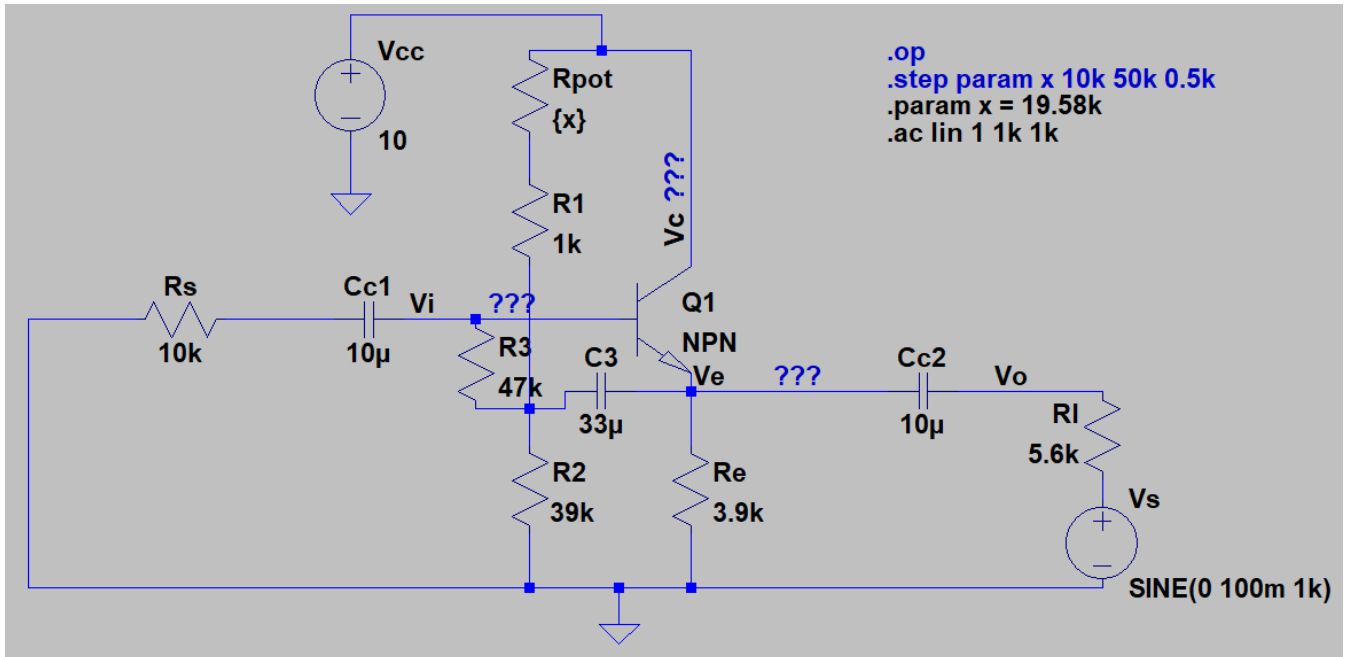

--- AC Analysis ---			
frequency:	1000	Hz	
V(vc):	mag: 0	phase: 0°	voltage
V(vi):	mag: 0.00173487	phase: 0.0777356°	voltage
V(ve):	mag: 0.00207381	phase: 0.0917466°	voltage
V(n001):	mag: 0.00197304	phase: 0.11322°	voltage
V(n003):	mag: 0.00207381	phase: 0.11322°	voltage
V(n004):	mag: 0.1	phase: 0°	voltage
V(vo):	mag: 0.00209274	phase: -7.55058°	voltage
V(n002):	mag: 0.00173487	phase: 0.168925°	voltage
Ic(Q1):	mag: 1.66276e-005	phase: -179.837°	device_current
Ib(Q1):	mag: 1.66276e-007	phase: -179.837°	device_current
Ie(Q1):	mag: 1.67938e-005	phase: 0.163463°	device_current
I(C3):	mag: 1.61154e-007	phase: 0.121348°	device_current
I(Cc1):	mag: 1.73487e-007	phase: 0.168925°	device_current
I(Cc2):	mag: 1.74867e-005	phase: 0.160894°	device_current
I(R3):	mag: 7.21147e-009	phase: -179.705°	device_current
I(Rs):	mag: 1.73487e-007	phase: 0.168925°	device_current
I(Rl):	mag: 1.74867e-005	phase: 0.160894°	device_current
I(Re):	mag: 5.31746e-007	phase: 0.0917466°	device_current
I(R2):	mag: 5.31746e-008	phase: 0.11322°	device_current
I(Rpot):	mag: 1.00768e-007	phase: -179.887°	device_current
I(R1):	mag: 1.00768e-007	phase: -179.887°	device_current
I(Vcc):	mag: 1.67283e-005	phase: 0.163161°	device_current
I(Vs):	mag: 1.74867e-005	phase: -179.839°	device_current

$$R_{out} = \frac{V_{out}}{I_{out}} = \frac{V(vo)}{I(Vs)} = \frac{0.00209274}{1.74867 \times 10^{-5}} = 119.676 \Omega$$

Observations and Conclusions

1. The common collector configuration approximately gives the same amplitude of output waveform as the input waveform, shifted by a DC offset. Hence, it is also called emitter follower and acts as level shifter.
2. The main advantage of Darlington pair over Common collector topology is that it gives a higher current gain because of cascading of two BJTs, which multiplies their h_{FE} (or β -value).
3. Bootstrap configuration is used to get high input impedance as the input impedance of the other two configurations contribute to loading effects which can be seen in their waveforms (120 mV peak-to-peak). The Bootstrap configuration however has a much higher input resistance and gives nearly the same waveform as the source voltage (gives 190 mV peak-to-peak while source has 200 mV peak-to-peak).
4. The output resistance of all the three configurations is low which is a desired characteristic of an amplifier.
5. The purpose of all the three amplifiers is to shift the DC offset of input while keeping the amplitude same at input and output terminals.
6. The best amplifier for voltage level shift is the bootstrap configuration since the source voltage is least attenuated due to loading at BJT input.
7. The best amplifier for high current gain is Darlington configuration due to two cascaded BJTs.