

## Lab V

### **Study of Instrumentation Amplifier using LM741**

#### Objectives

To study the Instrumentation Amplifier using op-amp LM741 and find out


1. Value of resistance ( $R_f$ ) for DC null point,
  2. Common mode gain ( $A_{cm}$ ) for the instrumentation amplifier,
  3. Differential mode gain ( $A_{dm}$ ) for the instrumentation amplifier
- and find
- a) the common mode rejection ratio (CMRR) for the instrumentation amplifier,
  - b) compare the results from simulation with the theoretical values of the quantities.

Also, draw schematic for each case.
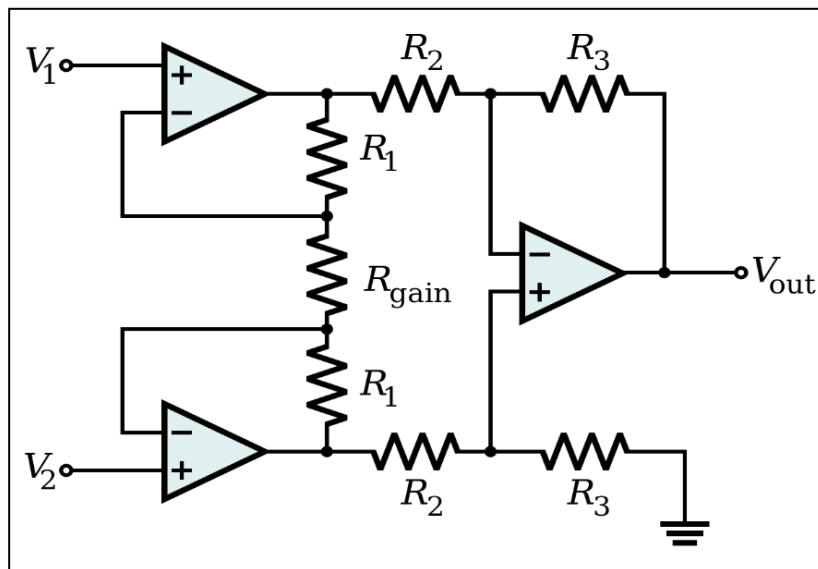
#### Instrumentation Amplifier




An **instrumentation amplifier** is a type of differential amplifier that has been outfitted with input buffer amplifiers, which eliminate the need for input impedance matching and thus make the amplifier particularly suitable for use in measurement and test equipment.

Additional characteristics include **very low DC offset**, **low drift**, **low noise**, **very high open-loop gain**, **very high common-mode rejection ratio**, and **very high input impedances**. Instrumentation amplifiers are used where great accuracy and stability of the circuit both short and long-term are required.


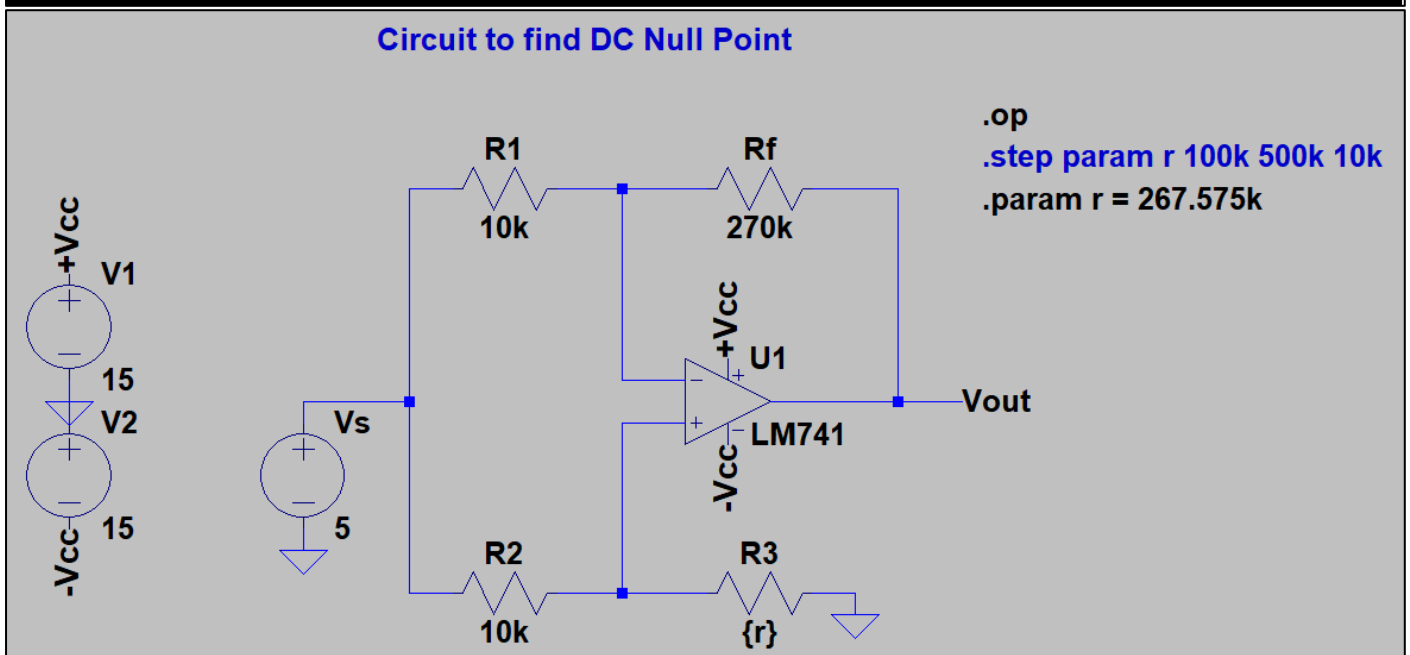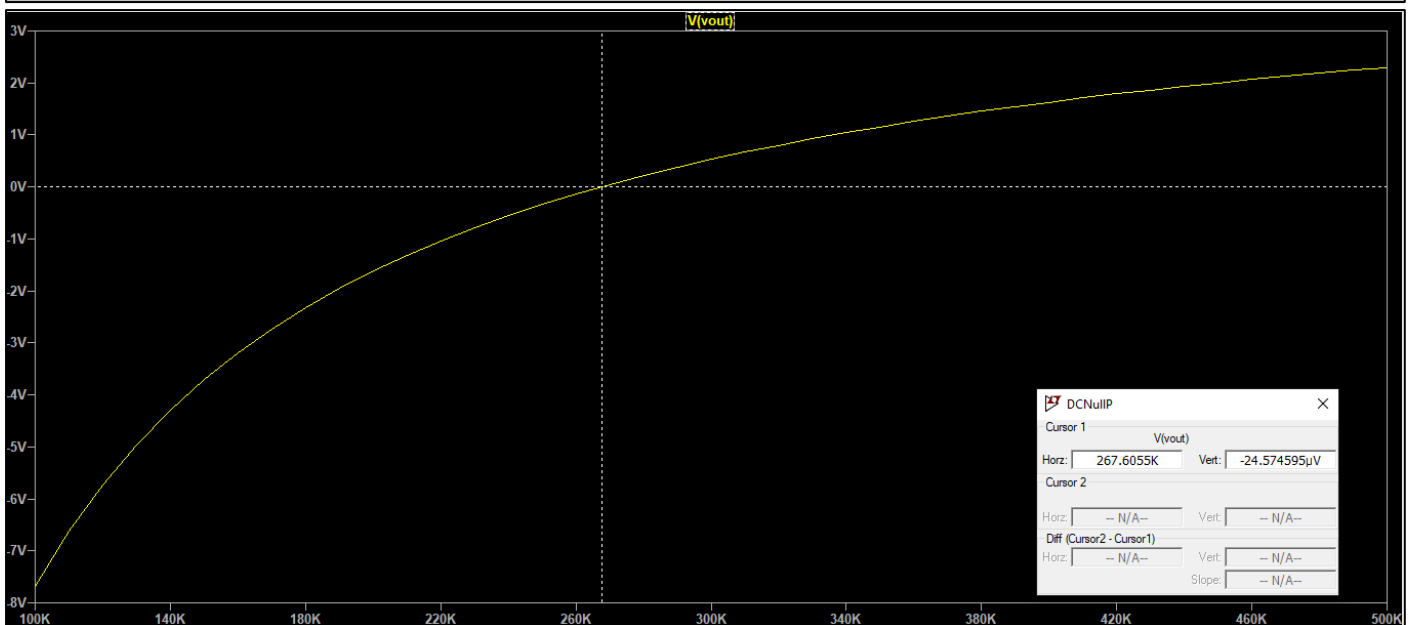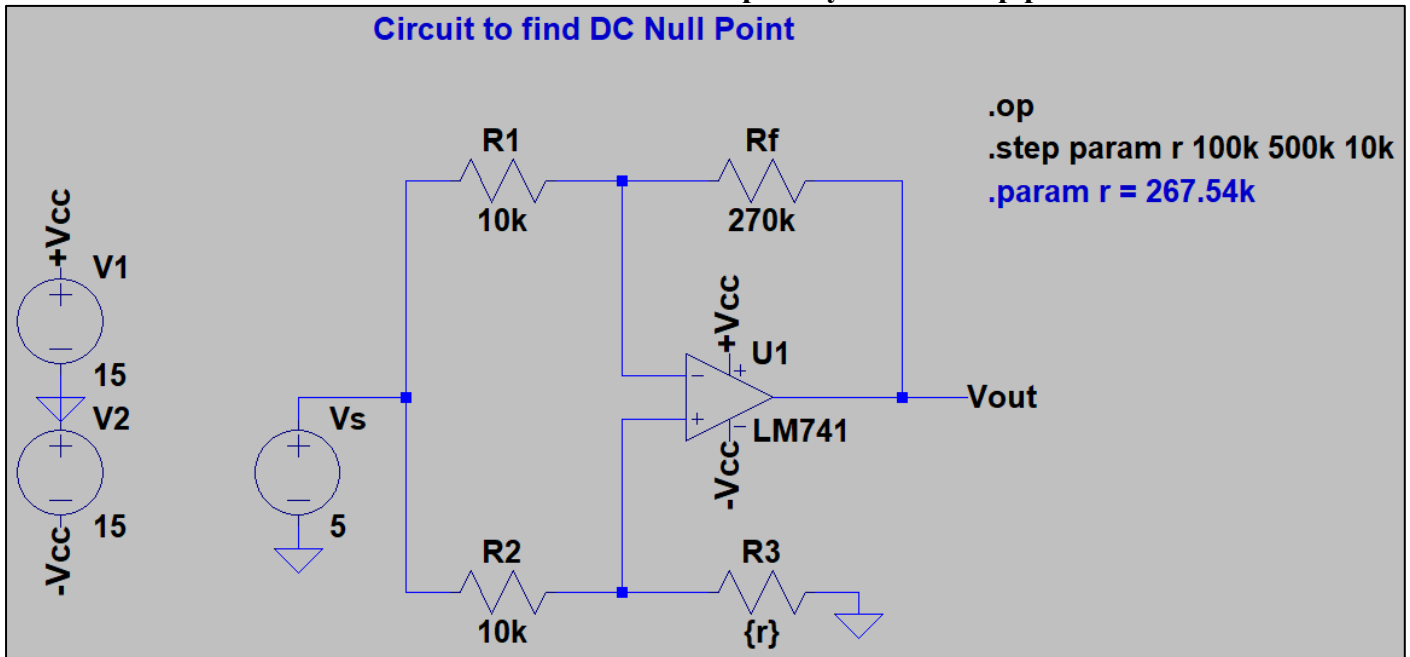
## 1. DC Null Point

Schematic and results from .op analysis with .step param




* H:\Academics\BITS\Year 4\4 - Semester 2\Analog Electronics\Labs\Lab 5\ASC Files\DCNullIP.asc		
--- Operating Point ---		
V(-vcc) :	-15	voltage
V(+vcc) :	15	voltage
V(n002) :	4.82047	voltage
V(n003) :	4.81931	voltage
V(vout) :	0.000635892	voltage
V(n001) :	5	voltage
I(Rf) :	-1.78512e-005	device_current
I(R3) :	-1.80111e-005	device_current
I(R2) :	-1.80686e-005	device_current
I(R1) :	-1.79534e-005	device_current
I(Vs) :	-3.6022e-005	device_current
I(V1) :	-0.00169262	device_current
I(V2) :	-0.00171063	device_current
Ix(u1:1) :	5.75579e-008	subckt_current
Ix(u1:2) :	1.02168e-007	subckt_current
Ix(u1:99) :	0.00169262	subckt_current
Ix(u1:50) :	-0.00171063	subckt_current
Ix(u1:28) :	1.78512e-005	subckt_current

## Results

The value of resistance  $R_f$  at DC null point ( $V_{out} = -9 \text{ nV} \approx 0\text{V}$ ) comes out to be approximately  $267.575 \text{ k}\Omega$ .

## 2. Common Mode Gain ( $A_{cm}$ )
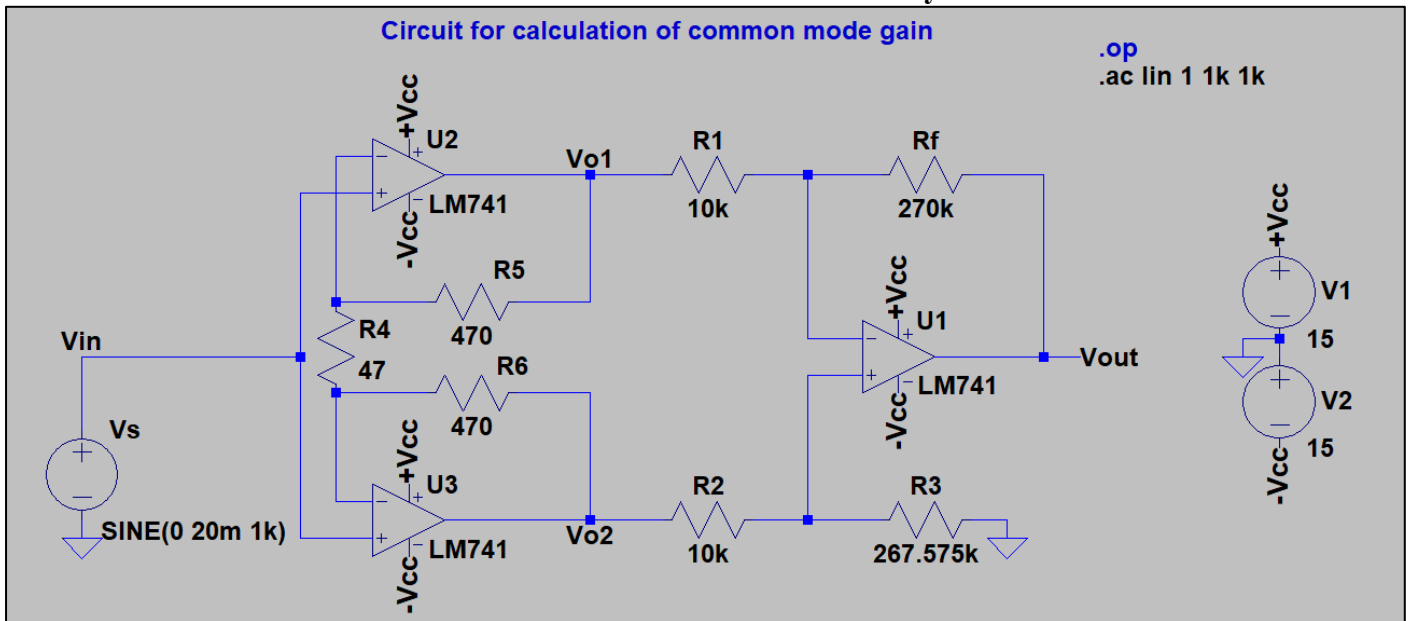
### Schematic and results from AC analysis



--- AC Analysis ---

frequency:	1000	Hz		
V(+vcc):	mag:	0	phase:	0°
V(-vcc):	mag:	0	phase:	0°
V(n002):	mag:	0.0192807	phase:	-0.0446846°
V(n003):	mag:	0.01928	phase:	-0.0512225°
V(vout):	mag:	0.000167774	phase:	157.483°
V(vo1):	mag:	0.0200005	phase:	-0.0513552°
V(vo2):	mag:	0.0200005	phase:	-0.051356°
V(n001):	mag:	0.0200005	phase:	-0.0512658°
V(vin):	mag:	0.02	phase:	0°
V(n004):	mag:	0.0200005	phase:	-0.0512658°
I(R4):	mag:	8.91015e-013	phase:	160.983°
I(R6):	mag:	6.69901e-011	phase:	-88.5106°
I(R5):	mag:	6.63868e-011	phase:	-89.9514°
I(Rf):	mag:	7.19845e-008	phase:	179.766°
I(R3):	mag:	7.20546e-008	phase:	179.949°
I(R2):	mag:	7.20531e-008	phase:	179.945°
I(R1):	mag:	7.1986e-008	phase:	179.77°
I(Vs):	mag:	1.33365e-010	phase:	-89.2621°
I(V2):	mag:	3.60105e-008	phase:	-0.157326°
I(V1):	mag:	3.6046e-008	phase:	179.843°
Ix(u1:1):	mag:	4.8737e-012	phase:	-107.112°
Ix(u1:2):	mag:	4.88516e-012	phase:	72.4558°
Ix(u1:99):	mag:	3.60236e-008	phase:	179.766°
Ix(u1:50):	mag:	3.5961e-008	phase:	179.766°
Ix(u1:28):	mag:	7.19845e-008	phase:	-0.233732°
Ix(u2:1):	mag:	6.66826e-011	phase:	90.7379°
Ix(u2:2):	mag:	6.66832e-011	phase:	-89.2278°
Ix(u2:99):	mag:	3.60066e-008	phase:	-0.282859°
Ix(u2:50):	mag:	3.59796e-008	phase:	-0.282859°
Ix(u2:28):	mag:	7.19863e-008	phase:	179.717°
Ix(u3:1):	mag:	6.66827e-011	phase:	90.738°
Ix(u3:2):	mag:	6.66832e-011	phase:	-89.2277°
Ix(u3:99):	mag:	3.6063e-008	phase:	-0.108177°
Ix(u3:50):	mag:	3.59919e-008	phase:	-0.108177°
Ix(u3:28):	mag:	7.2055e-008	phase:	179.892°

## Results

- The value of common mode gain from simulation comes out to be


$$A_{cm} = \frac{V_{out}}{V_{in}} = 8.387 \times 10^{-3} = -41.527 \text{ dB}$$

- The theoretical value of common mode gain should be

$$A_{cm} = 0$$

### 3. Differential Mode Gain $A_{dm}$
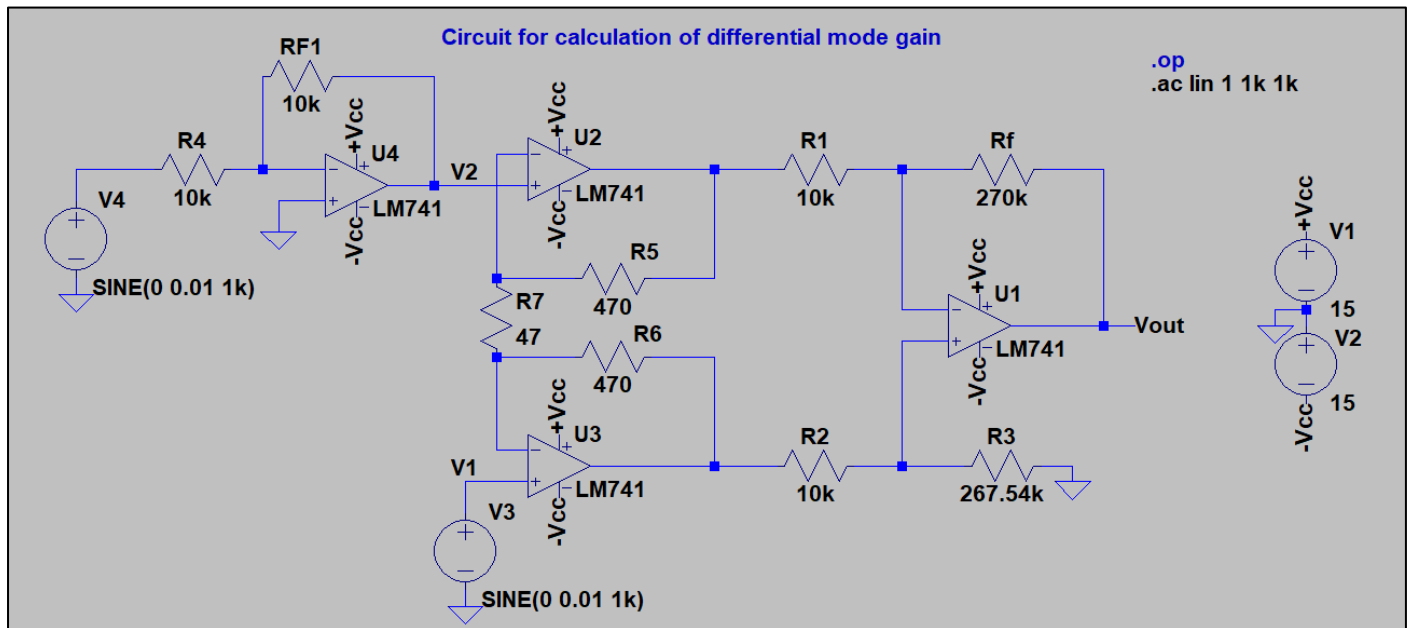
#### Schematic and results from AC analysis



\* H:\Academics\BITS\Year 4\4 - Semester 2\Analog Electronics\Labs\Lab 5\ASC Files\DMgain.asc

--- AC Analysis ---

frequency:	1000	Hz		
V(+vcc):	mag:	0	phase:	0°
V(-vcc):	mag:	0	phase:	0°
V(n005):	mag:	0.202269	phase:	-4.99967°
V(n006):	mag:	0.202315	phase:	-1.79694°
V(vout):	mag:	11.3258	phase:	-3.40151°
V(n004):	mag:	0.20989	phase:	178.305°
V(n008):	mag:	0.20989	phase:	-1.68752°
V(n001):	mag:	0.0099949	phase:	178.232°
V(v2):	mag:	0.00999989	phase:	179.881°
V(n007):	mag:	0.00999468	phase:	-1.61445°
V(v1):	mag:	0.01	phase:	0°
V(n002):	mag:	0.01	phase:	0°
V(n003):	mag:	1.01772e-005	phase:	89.6243°
I(R4):	mag:	9.99994e-007	phase:	179.942°
I(Rf1):	mag:	9.99994e-007	phase:	179.94°
I(R7):	mag:	0.00042531	phase:	178.309°
I(R6):	mag:	0.00042531	phase:	-1.69117°
I(R5):	mag:	0.00042531	phase:	178.309°
I(Rf):	mag:	4.11986e-005	phase:	-3.37245°
I(R3):	mag:	7.56204e-007	phase:	178.203°
I(R2):	mag:	7.58558e-007	phase:	-178.768°
I(R1):	mag:	4.11988e-005	phase:	-3.31668°
I(V4):	mag:	9.99994e-007	phase:	179.942°
I(V3):	mag:	1.00013e-009	phase:	-91.916°
I(V2):	mag:	0.00017082	phase:	-1.77912°
I(V1):	mag:	0.000171064	phase:	-1.76866°
Ix(u1:1):	mag:	4.0103e-008	phase:	86.3541°
Ix(u1:2):	mag:	4.0103e-008	phase:	-93.6454°
Ix(u1:99):	mag:	1.98338e-005	phase:	-3.37245°
Ix(u1:50):	mag:	2.13648e-005	phase:	-3.37245°
Ix(u1:28):	mag:	4.11986e-005	phase:	176.628°
Ix(u2:1):	mag:	1.02144e-009	phase:	-91.9625°
Ix(u2:2):	mag:	1.02144e-009	phase:	88.0386°
Ix(u2:99):	mag:	0.000325609	phase:	178.165°
Ix(u2:50):	mag:	0.000140884	phase:	178.165°
Ix(u2:28):	mag:	0.000466493	phase:	-1.83472°
Ix(u3:1):	mag:	1.00013e-009	phase:	88.084°
Ix(u3:2):	mag:	1.00013e-009	phase:	-91.9149°
Ix(u3:99):	mag:	0.00013522	phase:	-1.68597°
Ix(u3:50):	mag:	0.000290847	phase:	-1.68597°

## Results

- The value of differential mode gain from simulation comes out to be

$$A_{dm} = V_{out} / (V_1 - V_2) = 566.29 = 55.06 \text{ dB}$$

- The theoretical value of differential mode gain should be

$$A_{dm} = \left(1 + \frac{2R_5}{R_7}\right) \frac{R_F}{R_1} = 567 = 55.07 \text{ dB}$$

## Calculation of CMRR

The simulated value of common mode rejection ratio (CMRR) is:

$$\frac{A_{dm}}{A_{cm}} = \frac{566.29}{8.387 \times 10^{-3}} = 67519.97 = 96.58 \text{ dB}$$

The theoretical value of CMRR is: infinity.

## Conclusions

Hence, practical circuits like the instrumentation amplifier using LM 741 do not have ideal infinite CMRR but are limited to some finite large value due to mismatch. The theoretical value of CMRR is much higher than simulated value as per calculations.