

Name: Swagat Panda ID: 2017B5A30983P

Lab III

Inverting mode, Non-inverting mode, Adder, Subtractor using LM741

Objectives

To study the basic configuration of OPAMP (LM-741)

1. Inverting mode
2. Non-inverting mode
3. Adder
4. Subtractor

and find



a) Simulated and theoretical values of voltage gain (A_v) and input-output voltage waveforms with magnitude for inverting and non-inverting mode,

b) Simulated and theoretical values of output voltage (V_o) for adder and subtractor,

Also, record observations and write conclusions for each amplifier configuration.

IC LM741

- LM741 operational amplifier is a DC-coupled high gain electronic voltage amplifier.
- It has only one op-amp inside.
- An operational amplifier IC is used as a comparator, which compares the two signals, the inverting and non-inverting signal.
- The main function of this IC is to do mathematical operation in various circuits.
- Op-amps have large gain and usually used as Voltage Amplifier.
- The LM741 can operate with a single or dual power supply voltage.

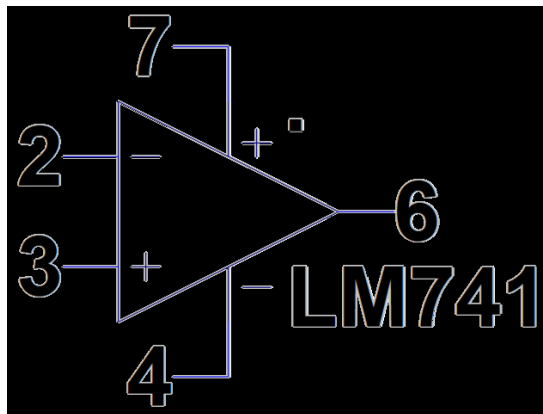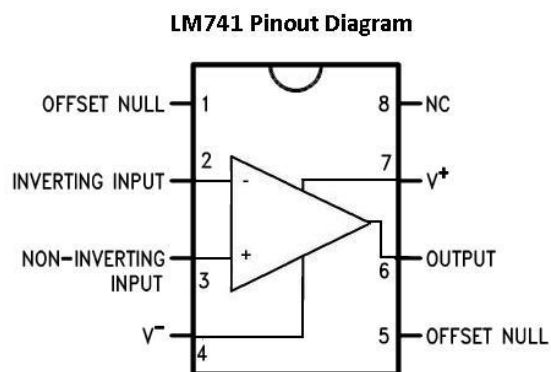

1. Inverting Mode – Schematic, .ac results and Waveforms

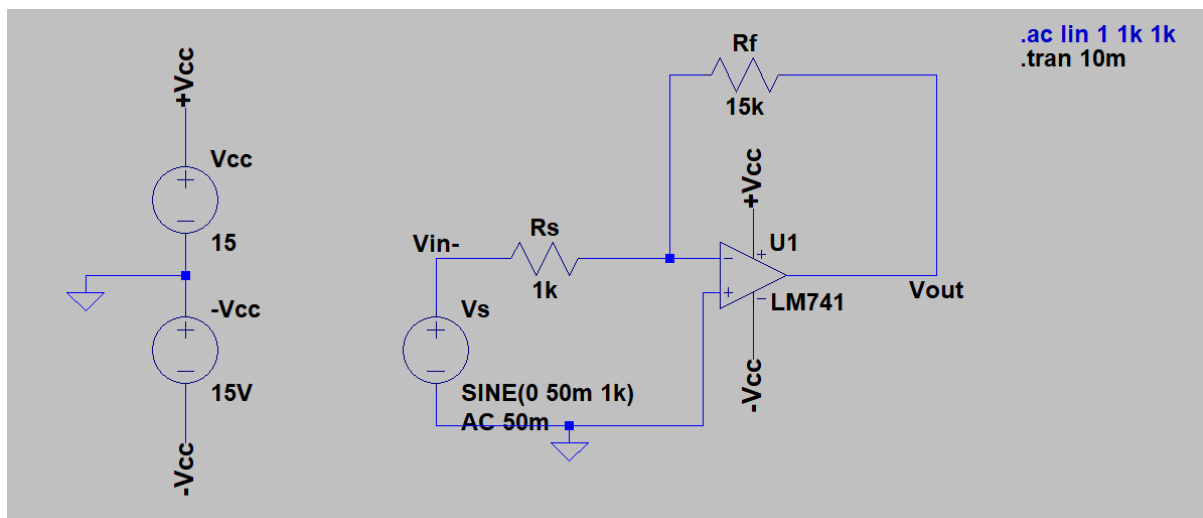


Fig 1.1 - Circuit diagram for Inverting Mode

* H:\Academics\BITS\Year 4\4 - Semester 2\Analog Electronics\Labs\Lab 3\ASC files\Inverting Mode.asc				
--- AC Analysis ---				
frequency:	1000	Hz		
V(n001):	mag: 0.000758591	phase: 88.8112°	voltage	
V(-vcc):	mag: 0	phase: 0°	voltage	
V(+vcc):	mag: 0	phase: 0°	voltage	
V(vout):	mag: 0.749846	phase: 179.07°	voltage	
V(n002):	mag: 0.05	phase: 0°	voltage	
I(Rs):	mag: 4.999e-005	phase: 179.131°	device_current	
I(Rf):	mag: 4.999e-005	phase: 179.128°	device_current	
I(-vcc):	mag: 2.48267e-005	phase: 179.128°	device_current	
I(Vcc):	mag: 2.51633e-005	phase: -0.872383°	device_current	
I(Vs):	mag: 4.999e-005	phase: 179.131°	device_current	
Ix(u1:1):	mag: 2.68845e-009	phase: -91.1901°	subckt_current	
Ix(u1:2):	mag: 2.68845e-009	phase: 88.8099°	subckt_current	
Ix(u1:99):	mag: 2.51633e-005	phase: 179.128°	subckt_current	
Ix(u1:50):	mag: 2.48267e-005	phase: 179.128°	subckt_current	
Ix(u1:28):	mag: 4.999e-005	phase: -0.872383°	subckt_current	

Fig 1.2 – AC Analysis for Inverting Mode

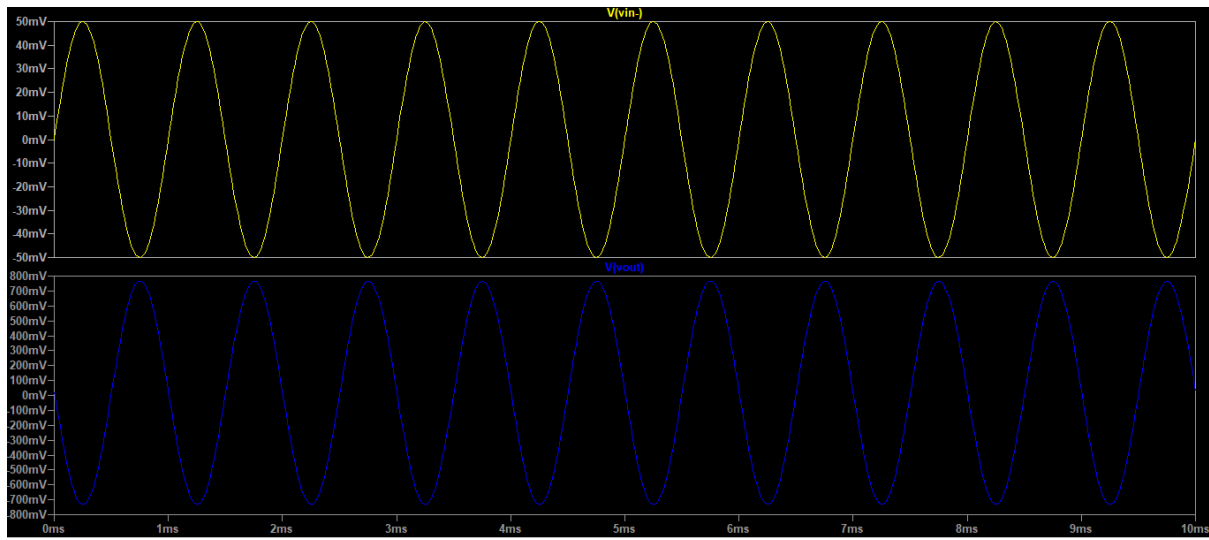


Fig 1.3- Input-Output waveform for Inverting Mode

Observations and Calculations

From Theory:

The output voltage for an inverting amplifier can be calculated using the formula

$$A_v = \frac{V_o}{V_s} = -\frac{R_F}{R_s}$$

As $|V_s| = 50\text{mV}$, so

$$|V_o| = \frac{15\text{k}\Omega}{1\text{k}\Omega} \times 50\text{mV} = 0.75\text{V}$$

Negative sign of A_v indicates phase shift by 180° . Hence, if V_s has 0° phase, the V_o must have 180° phase.

Voltage gain (A_v) = **-15**.

Simulated:

The amplitude of V_o comes out to be **0.749846V** with a phase of **179.07°**.

Voltage gain (A_v) = **-14.99692**.

Conclusions

- The amplitude and phase of simulated waveform are very close to the expected results.
- The waveform is inverted and amplified.
- The simulated results are not exactly equal to theoretical results because the Op-Amp LM741 IC is not an ideal Op-Amp. It draws very small current (in order of nA) at its input, does not have infinite input resistance and zero output resistance, and has a finite gain which are the main causes of deviation from the expected theoretical results.

2. Non - Inverting Mode – Schematic, .ac results and Waveforms

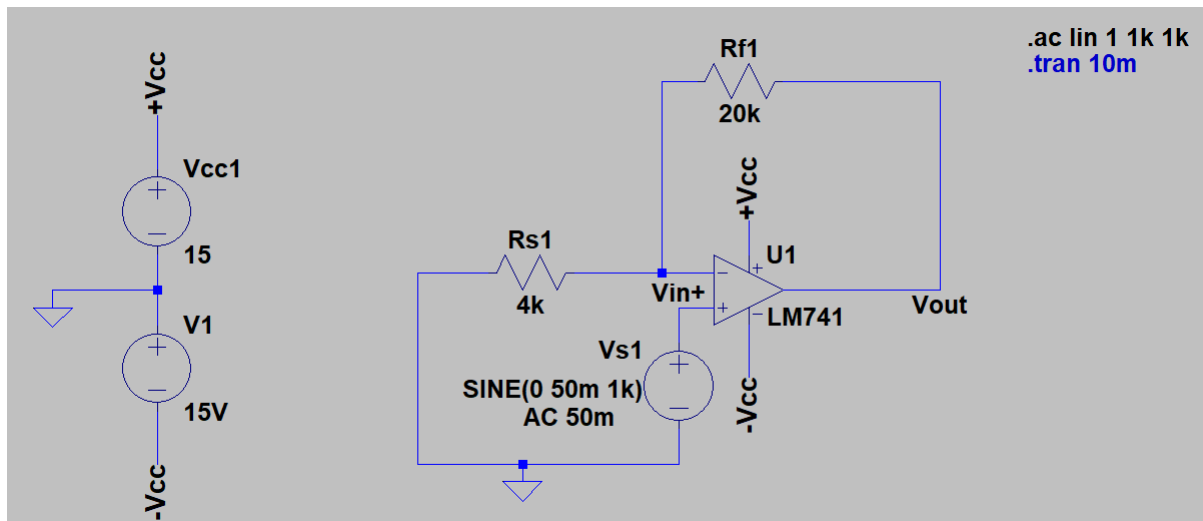


Fig 2.1- Circuit diagram for Non-Inverting Mode

* H:\Academics\BITS\Year 4\4 - Semester 2\Analog Electronics\Labs\Lab 3\ASC files\Non - Inverting Mode....

--- AC Analysis ---				
frequency:	1000	Hz		
V(n001):	mag: 0.0499993	phase: -0.340162°		voltage
V(vin+):	mag: 0.05	phase: 0°		voltage
V(-vcc):	mag: 0	phase: 0°		voltage
V(+vcc):	mag: 0	phase: 0°		voltage
V(vout):	mag: 0.299996	phase: -0.344212°		voltage
I(Rs1):	mag: 1.24998e-005	phase: -0.340162°		device_current
I(Rf1):	mag: 1.24998e-005	phase: -0.345022°		device_current
I(V1):	mag: 6.23647e-006	phase: -0.345022°		device_current
I(Vcc1):	mag: 6.26335e-006	phase: 179.655°		device_current
I(Vs1):	mag: 1.06018e-009	phase: -90.4425°		device_current
Ix(u1:1):	mag: 1.06018e-009	phase: 89.5575°		subckt_current
Ix(u1:2):	mag: 1.06017e-009	phase: -90.4371°		subckt_current
Ix(u1:99):	mag: 6.26335e-006	phase: -0.345022°		subckt_current
Ix(u1:50):	mag: 6.23647e-006	phase: -0.345022°		subckt_current
Ix(u1:28):	mag: 1.24998e-005	phase: 179.655°		subckt_current

Fig 2.2 – AC Analysis for Inverting Mode

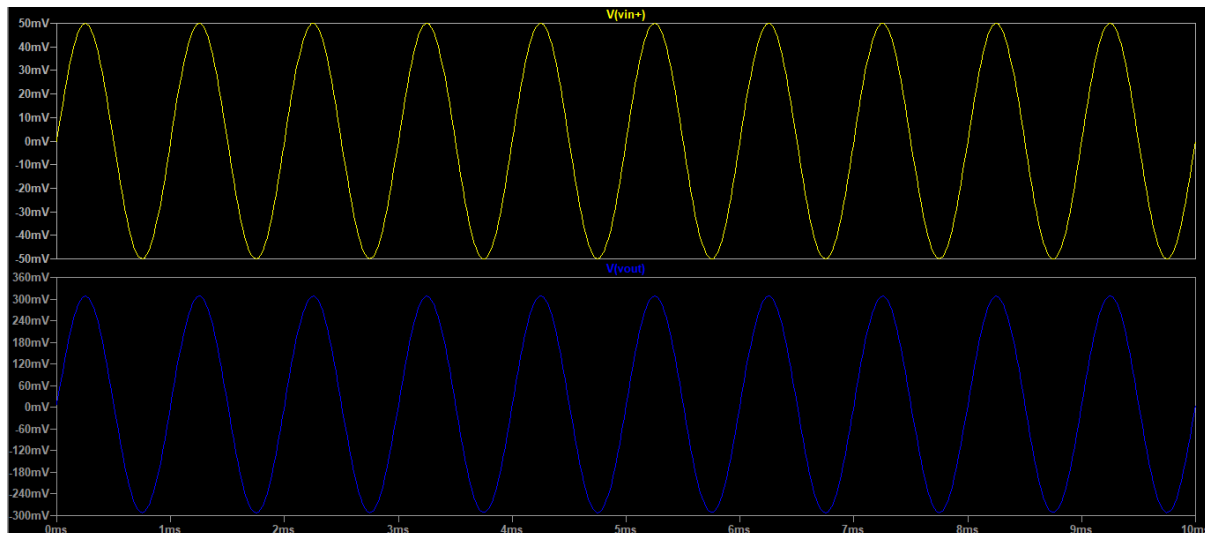


Fig 2.3 - Input-Output waveform for Non-Inverting Mode

Observations and Calculations

From Theory:

The output voltage for a non-inverting amplifier can be calculated using the formula

$$A_v = \frac{V_o}{V_s} = 1 + \frac{R_F}{R_s}$$

As $|V_s| = 50\text{mV}$, so

$$|V_o| = \left(1 + \frac{20\text{k}\Omega}{4\text{k}\Omega} \right) \times 50\text{mV} = 0.3\text{V}$$

Positive sign of A_v indicates no phase shift. Hence, if V_s has 0° phase, the V_o must have 0° phase.

Voltage gain (A_v) = 6.

Simulated:

The amplitude of V_o comes out to be **0.29996V** with a phase of **-0.34212°**.

Voltage gain (A_v) = **5.99992**.

Conclusions

- The amplitude and phase of simulated waveform are very close to the expected results.
- The waveform is amplified and remains in phase.
- The simulated results are not exactly equal to theoretical results because the Op-Amp LM741 IC is not an ideal Op-Amp. It draws very small current (in order of nA) at its input, does not have infinite input resistance and zero output resistance, and has a finite gain which are the main causes of deviation from the expected theoretical results.

3. Adder – Schematic, .ac results and Waveforms

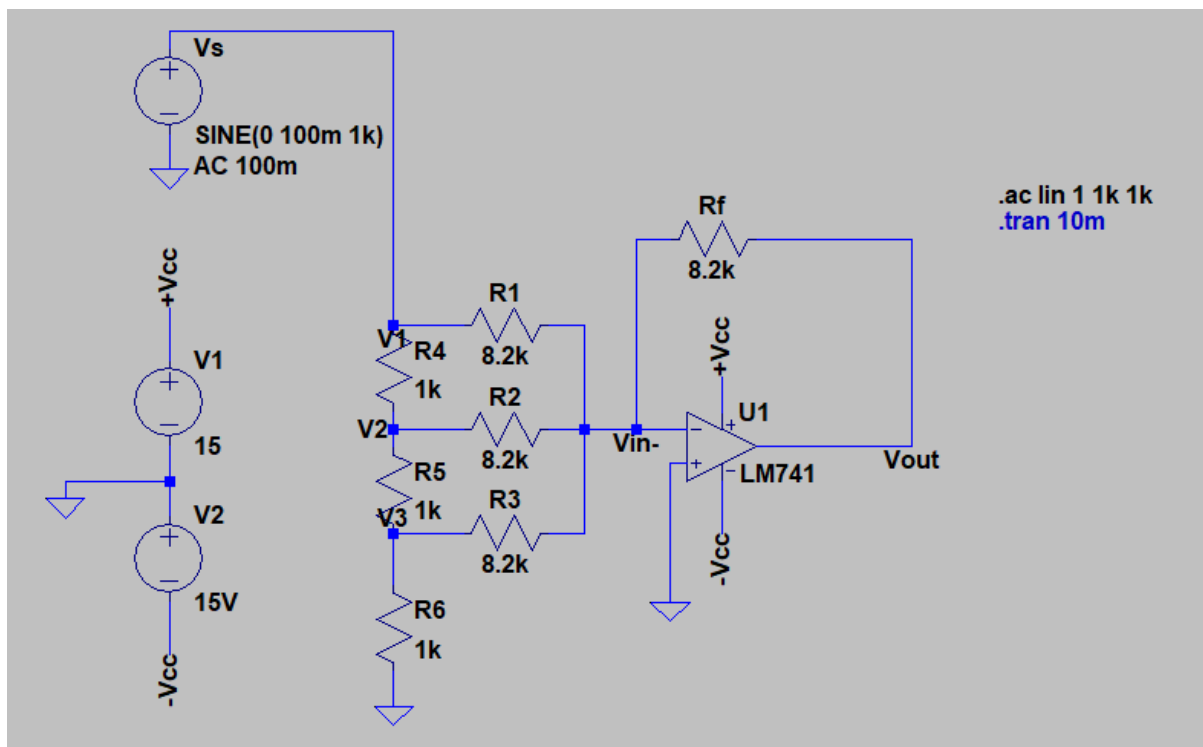


Fig 3.1 - Circuit diagram for Adder

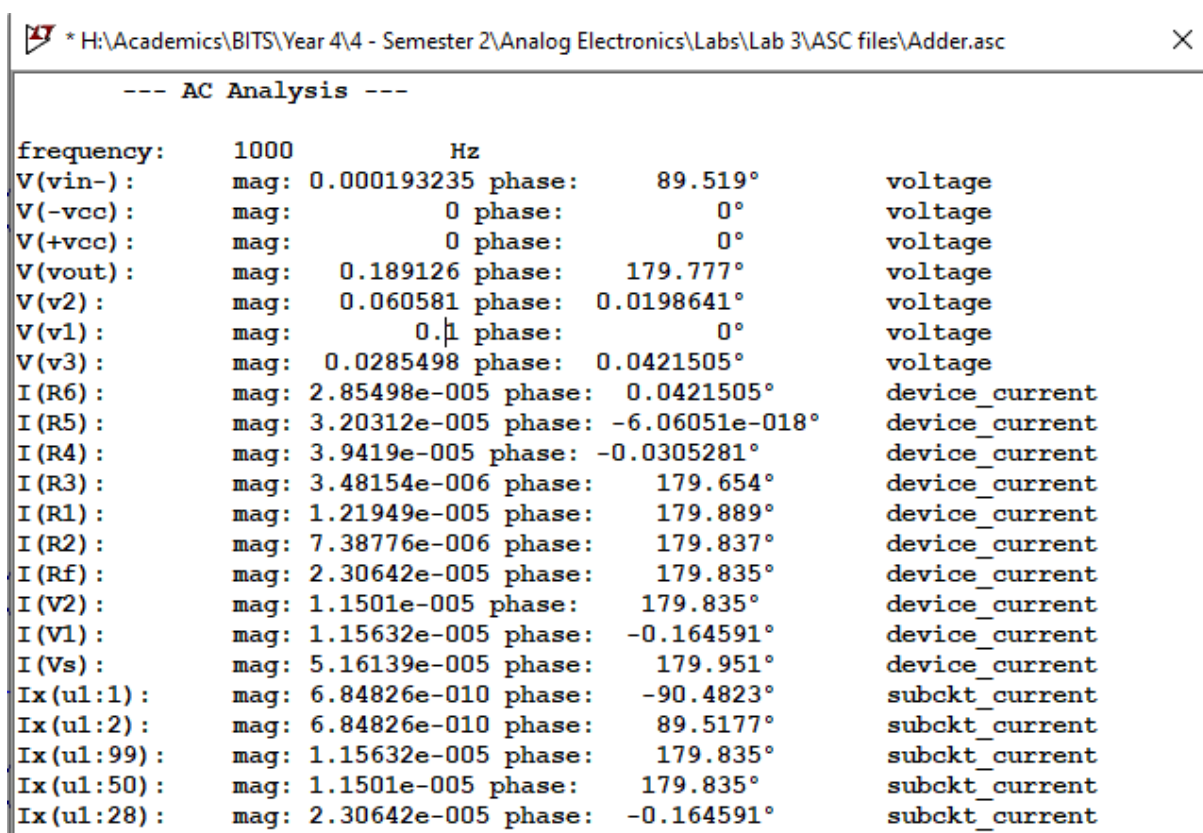


Fig 3.2 - AC Analysis for Adder

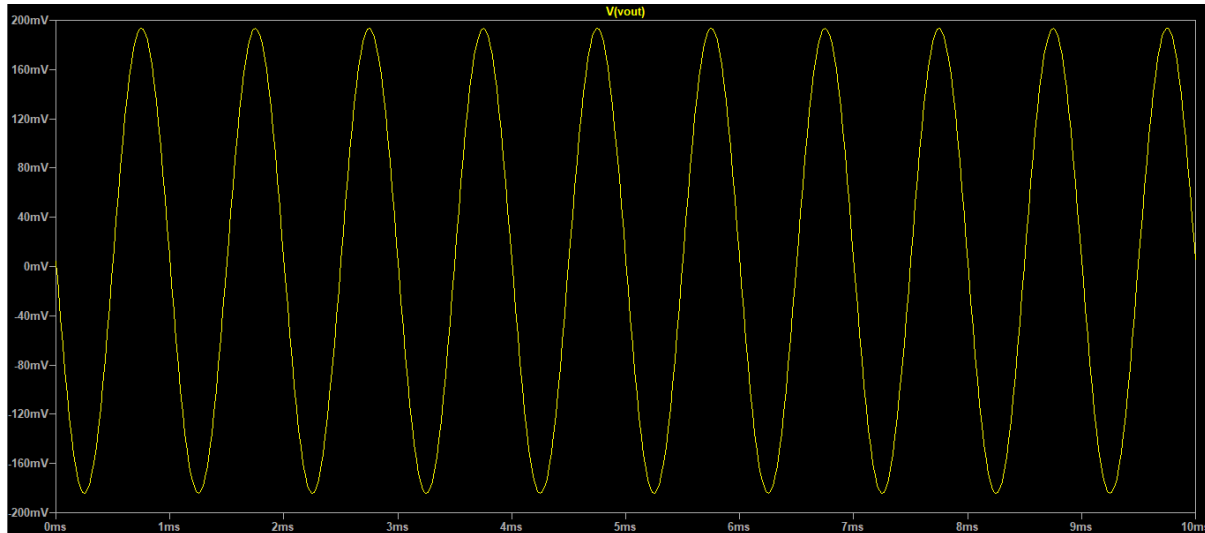


Fig 3.3 - Input-Output waveform for Adder

Observations and Calculations

From Theory:

The output voltage for a summing amplifier (adder) can be calculated using the formula

$$V_o = - \left(\frac{R_F}{R_1} V_1 + \frac{R_F}{R_2} V_2 + \frac{R_F}{R_3} V_3 \right)$$

As $|V_s| = 100 \text{ mV}$, so from the values obtained we have

$$V_s = V_1 = 100 \text{ mV}$$

$$V_2 = 60.581 \text{ mV}$$

$$V_3 = 28.5498 \text{ mV}$$

hence

$$|V_o| = \left(\frac{8.2 \text{ k}\Omega}{8.2 \text{ k}\Omega} \times 100 \text{ mV} + \frac{8.2 \text{ k}\Omega}{8.2 \text{ k}\Omega} \times 60.581 \text{ mV} + \frac{8.2 \text{ k}\Omega}{8.2 \text{ k}\Omega} \times 28.5498 \text{ mV} \right) = 189.13 \text{ mV}$$

Negative sign of A_v indicates phase shift of 180° . Hence, if V_s has 0° phase, the V_o must have 180° phase.

Simulated:

The amplitude of V_o comes out to be **0.1892V** with a phase of **179.77°**.

Conclusions

- The amplitude and phase of simulated waveform are very close to the expected results.
- The waveform is inverted and has a higher magnitude than the input voltages.
- The simulated results are not exactly equal to theoretical results because the Op-Amp LM741 IC is not an ideal Op-Amp. It draws very small current (in order of nano Amperes) at its input, does not have infinite input resistance and zero output resistance, and has a finite gain which are the main causes of deviation from the expected theoretical results.
- If by error, we apply voltage division ignoring R_1 , R_2 and R_3 , then the theoretical results are very different from the results from simulation. Hence, we should use values of V_1 , V_2 and V_3 from the analysis itself for theoretical calculations.

4. Subtractor – Schematic, .ac results and Waveforms

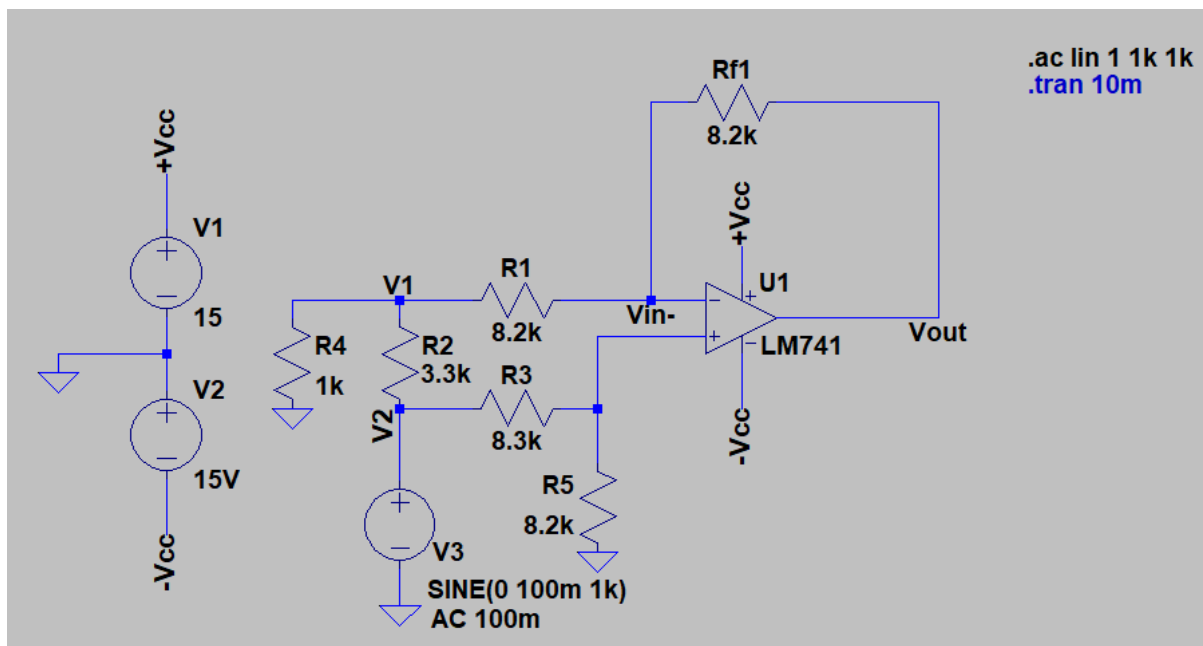


Fig 4.1 - Circuit diagram for Subtractor

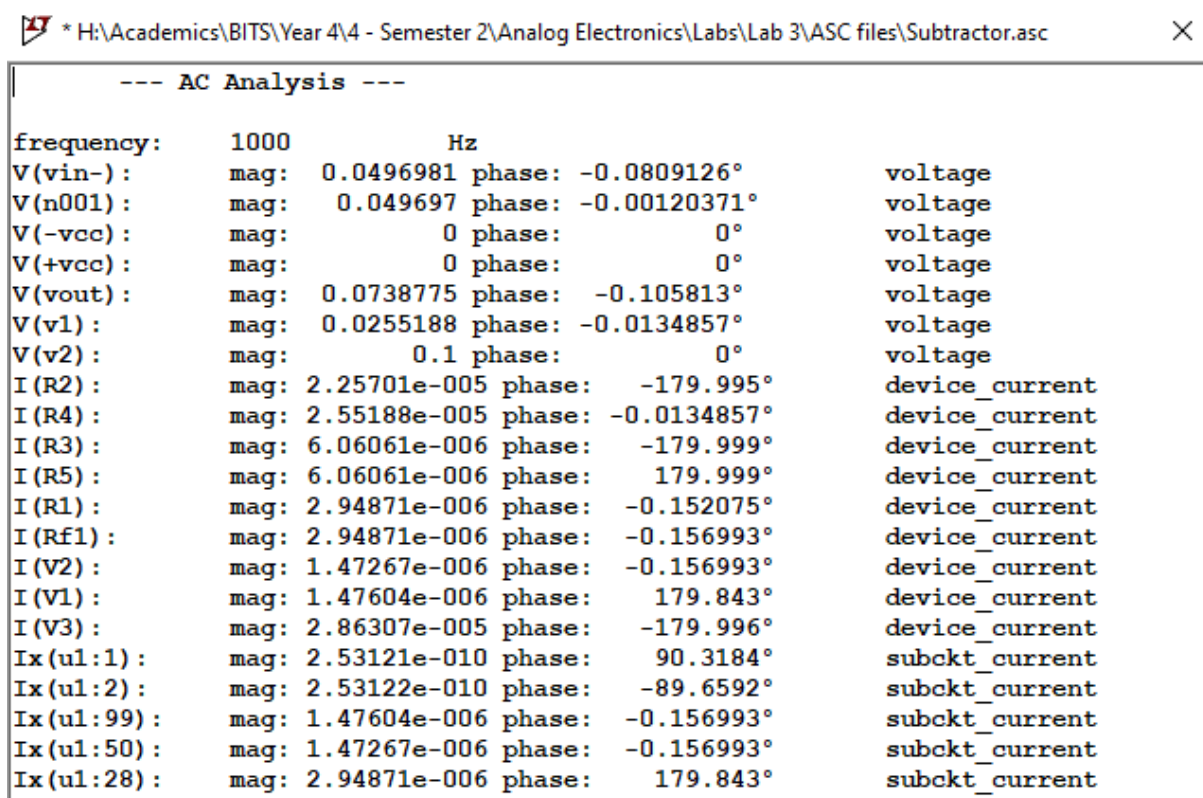


Fig 4.2 - Analysis for Subtractor

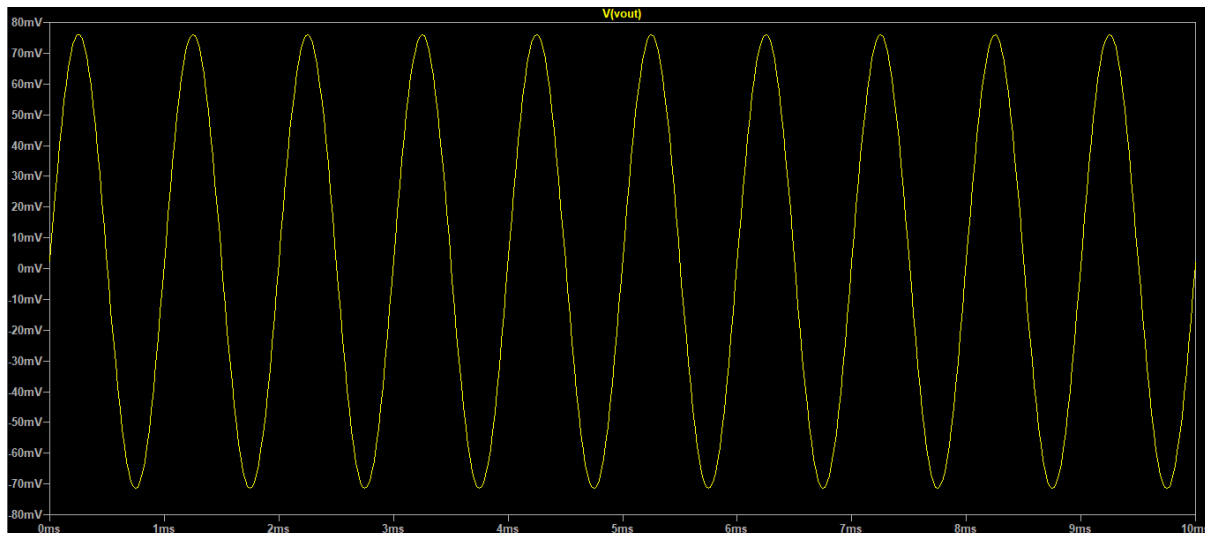


Fig 4.3 - Input-Output waveform for Subtractor

Observations and Calculations

From Theory:

The output voltage for a difference amplifier (subtractor) can be calculated using the formula

$$V_o = \frac{R_F}{R_1}(V_1 - V_2)$$

As $|V_s| = 100 \text{ mV}$, so from the values obtained we have

$$V_1 = 25.5118 \text{ mV}$$

$$V_s = V_2 = 100 \text{ mV}$$

$$\Rightarrow |V_o| = \frac{8.2 \text{ k}\Omega}{8.2 \text{ k}\Omega} \times (100 - 25.5118) = 74.4882 \text{ mV}$$

Positive sign of A_v indicates no phase shift. Hence, if V_s has 0° phase, the V_o must have 0° phase.

Simulated:

The amplitude of V_o comes out to be **0.0738775 V** with a phase of **-0.1058°**.

Conclusions

- The amplitude and phase of simulated waveform is very close to the expected results.
- The waveform is amplified with respect to difference of the voltages V_1 and V_2 and remains in phase.
- The simulated results are not exactly equal to theoretical results because the Op-Amp LM741 IC is not an ideal Op-Amp. It draws very small current (in order of nano Amperes) at its input, does not have infinite input resistance and zero output resistance, and has a finite gain which are the main causes of deviation from the expected theoretical results.
- If by error, we apply voltage division ignoring R_1 and R_2 , then the theoretical results are very different from the results from simulation. Hence, we should use values of V_1 and V_2 from the analysis itself for theoretical calculations.

Results

S.No	Configuration	Simulated Value	Theoretical Value
1	Inverting mode	$A_v = -14.99692$	$A_v = -15$
2	Non-Inverting mode	$A_v = 5.9992$	$A_v = 6$
3	Adder	$V_{out} = 0.189126 \text{ V}$	$V_{out} = 0.18913 \text{ V}$
4	Subtractor	$V_{out} = 0.0738775 \text{ V}$	$V_{out} = 0.0744882 \text{ V}$