

Name: Swagat Panda
ID: 2017B5A30983P

Lab 8

Study the sinusoidal and non-sinusoidal oscillators using LM741

Objectives

To study the sinusoidal and non-sinusoidal oscillators using op-amp IC LM741


1. RC phase shift oscillator
2. Wein Bridge oscillator

and draw output waveforms in each case.


Also draw the schematic for each filter and compare theoretical values with simulated ones.

Oscillator Circuits

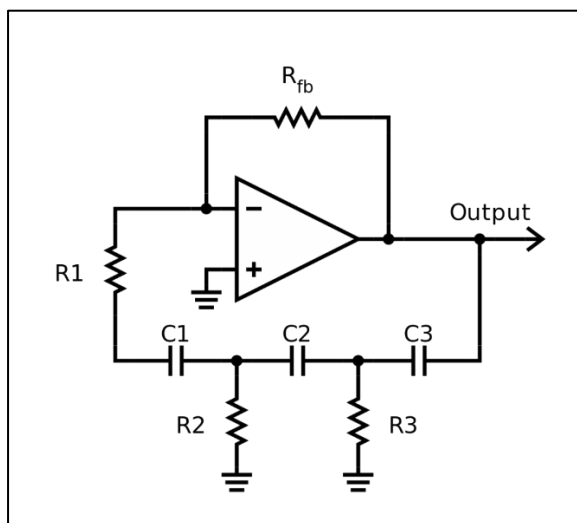An **oscillator** is a circuit which produces a continuous, repeated, alternating waveform without any input. Oscillators basically convert unidirectional current flow from a DC source into an alternating waveform which is of the desired frequency, as decided by its circuit components.



RC Phase Shift Oscillator


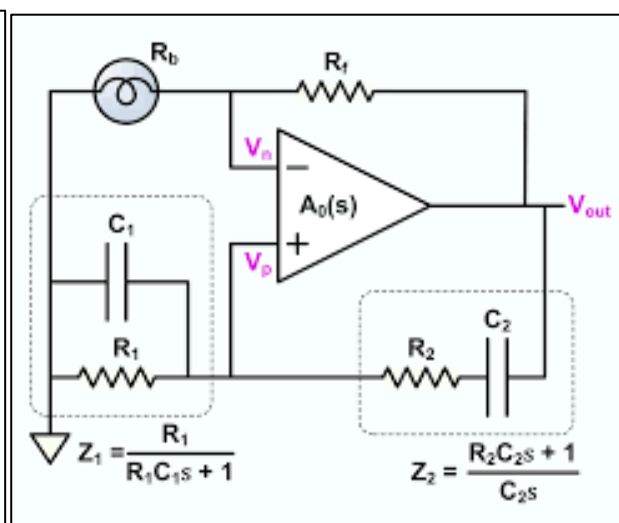


Wein Bridge Oscillator

1. RC Phase Shift Oscillator



$$C = 0.1\mu\text{F}$$

Schematic and Waveform

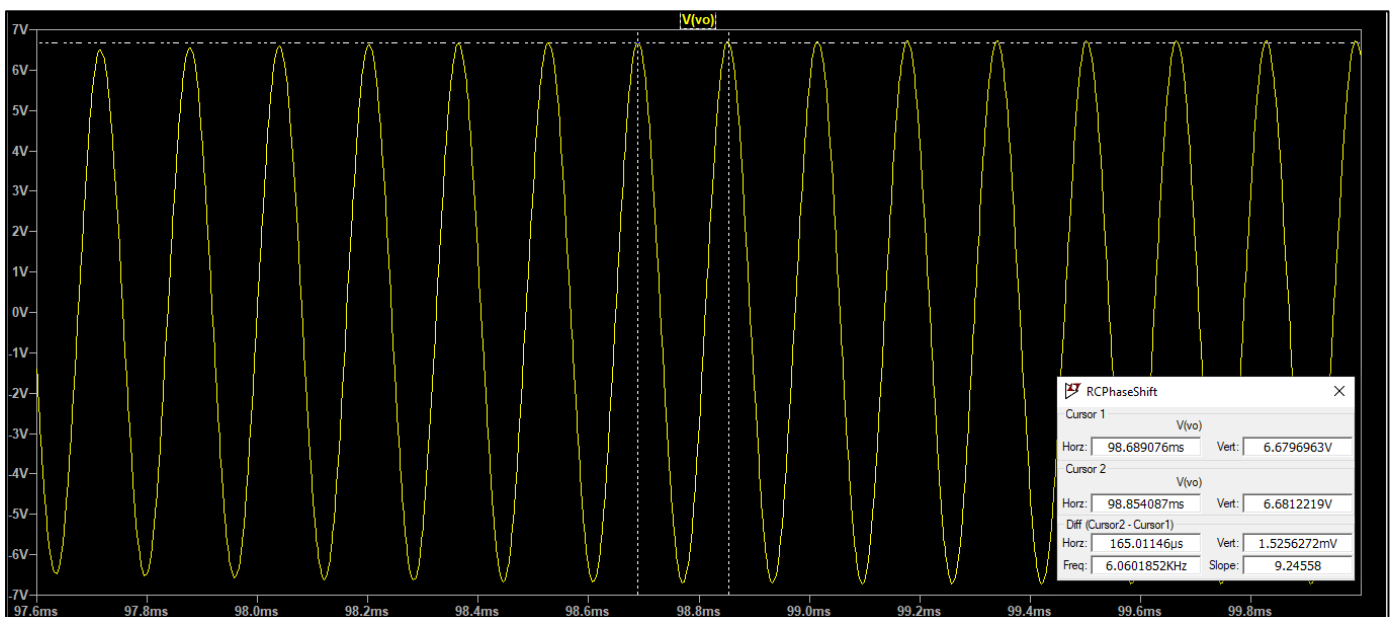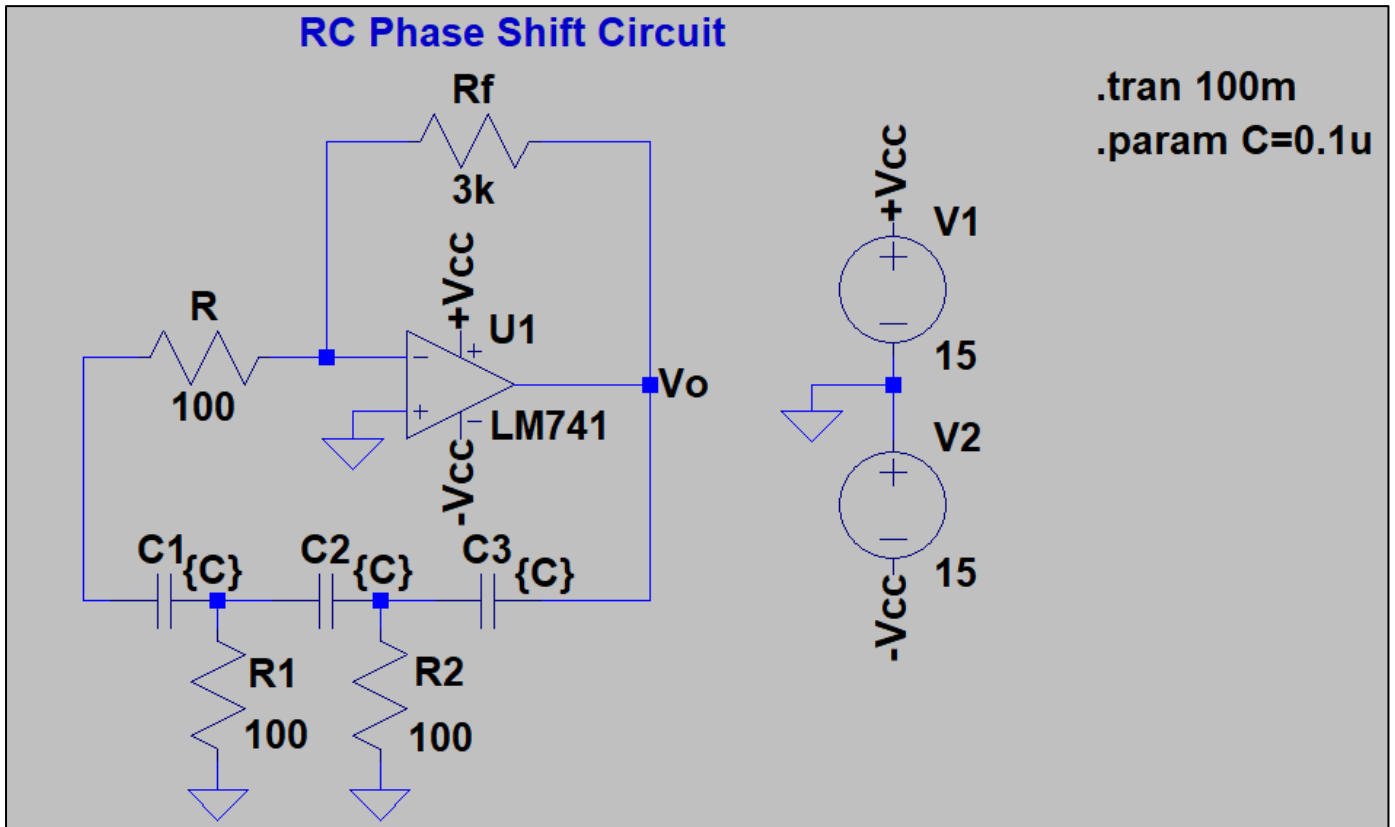

$$C = 0.2\mu\text{F}$$



Schematic and Waveform

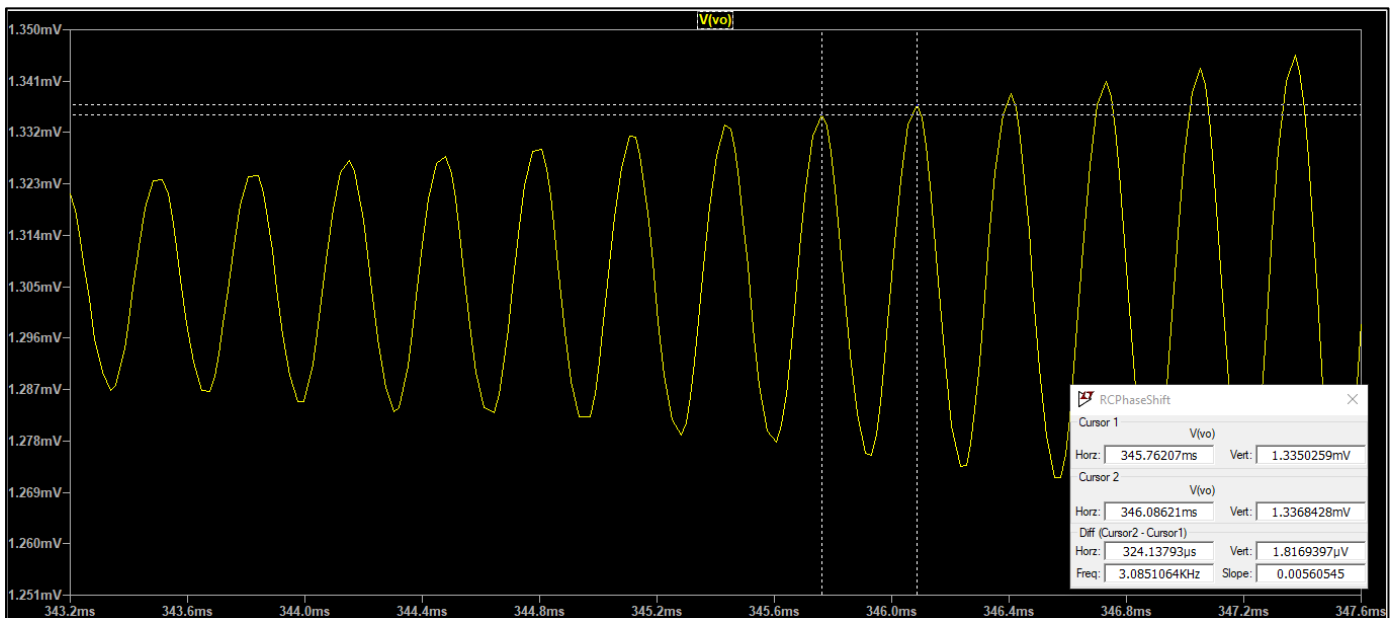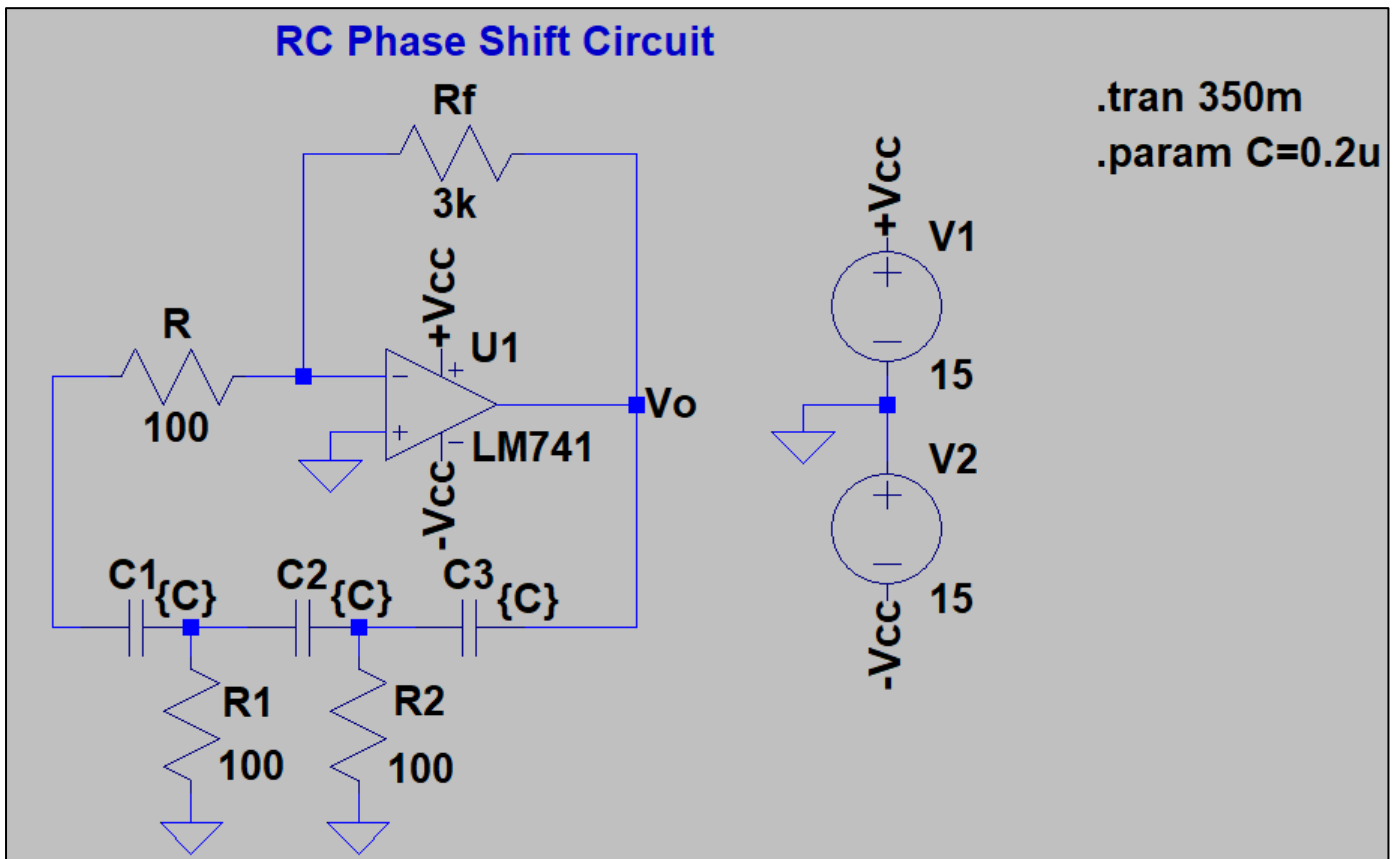

2. Wein Bridge Oscillator



$$C = 0.1\mu\text{F}$$

Schematic and Waveforms

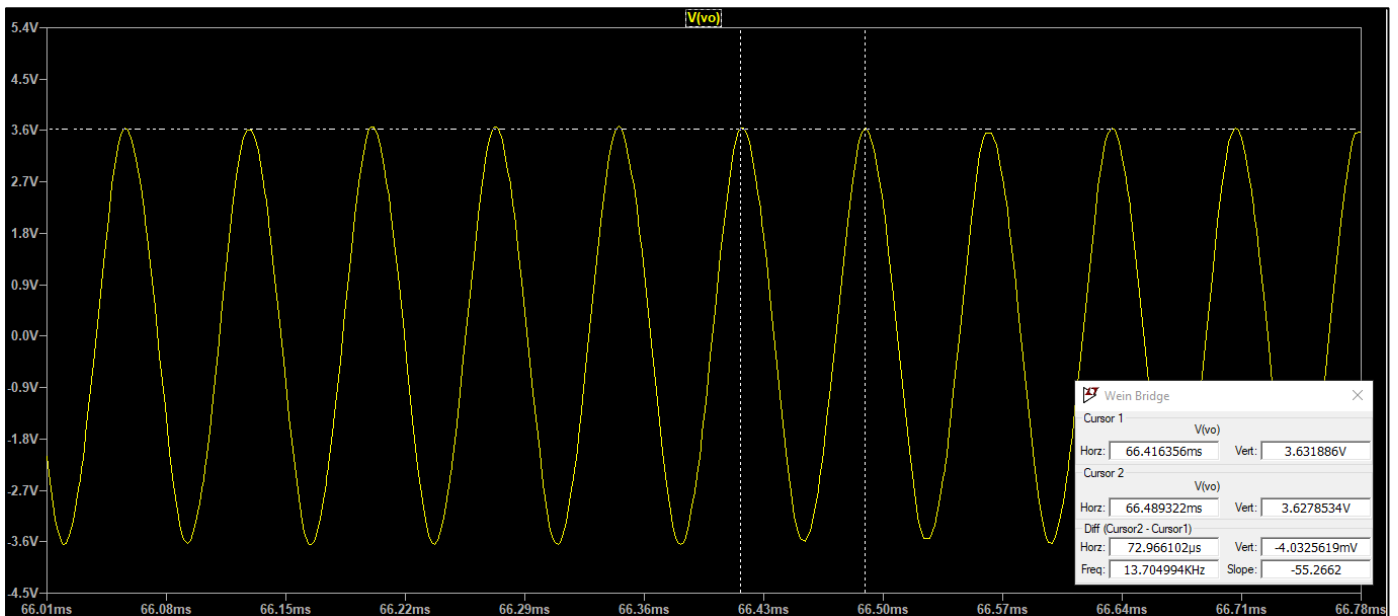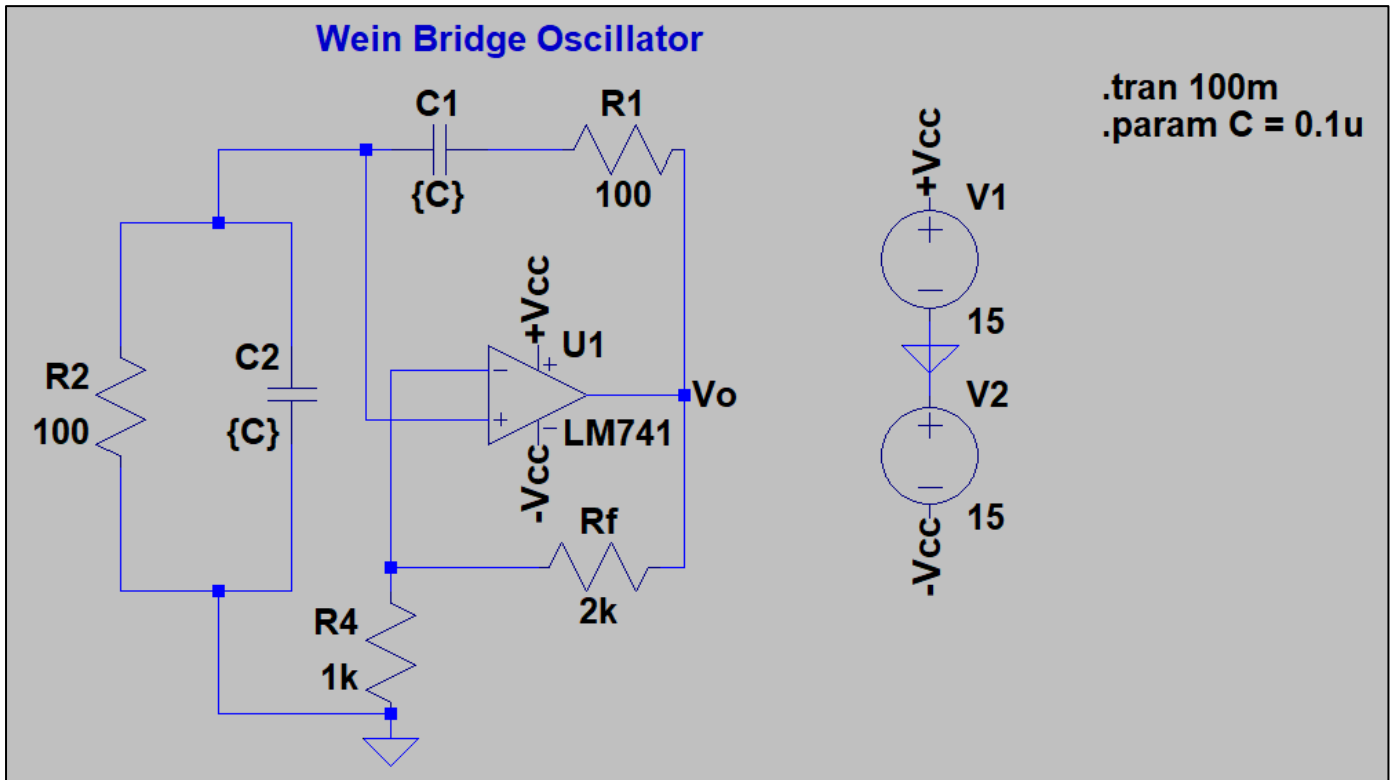

$$C = 0.2\mu F$$

Schematic and Waveforms

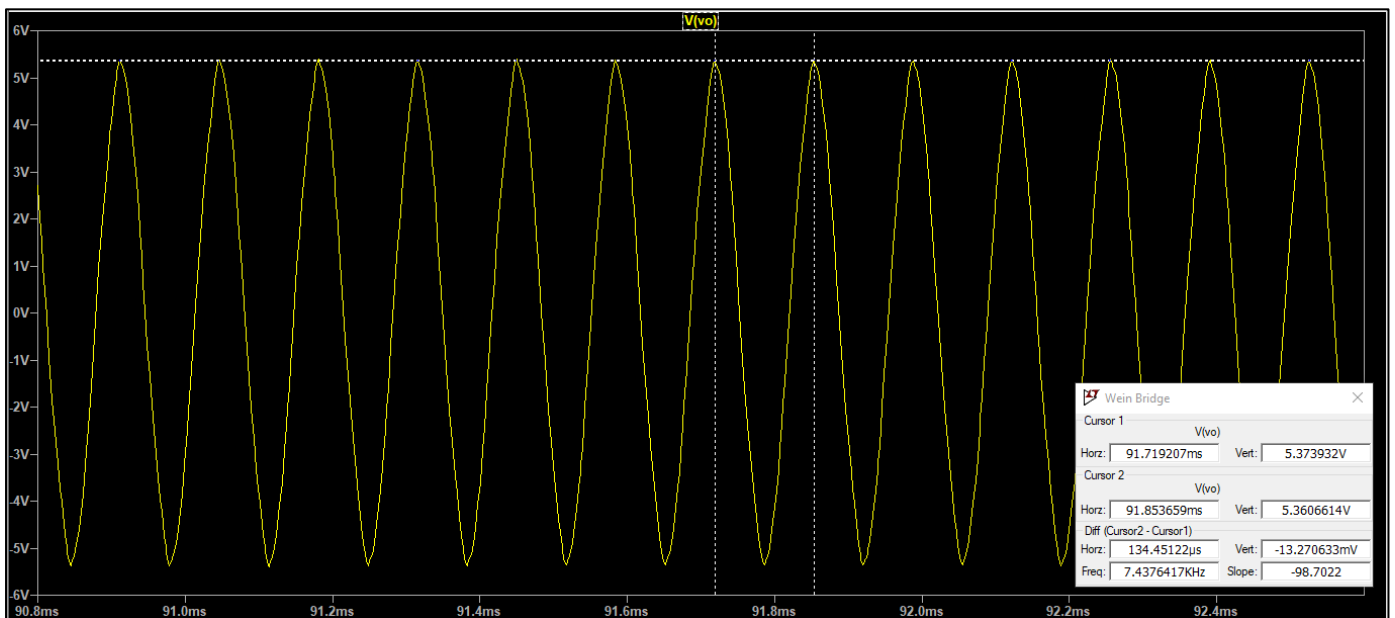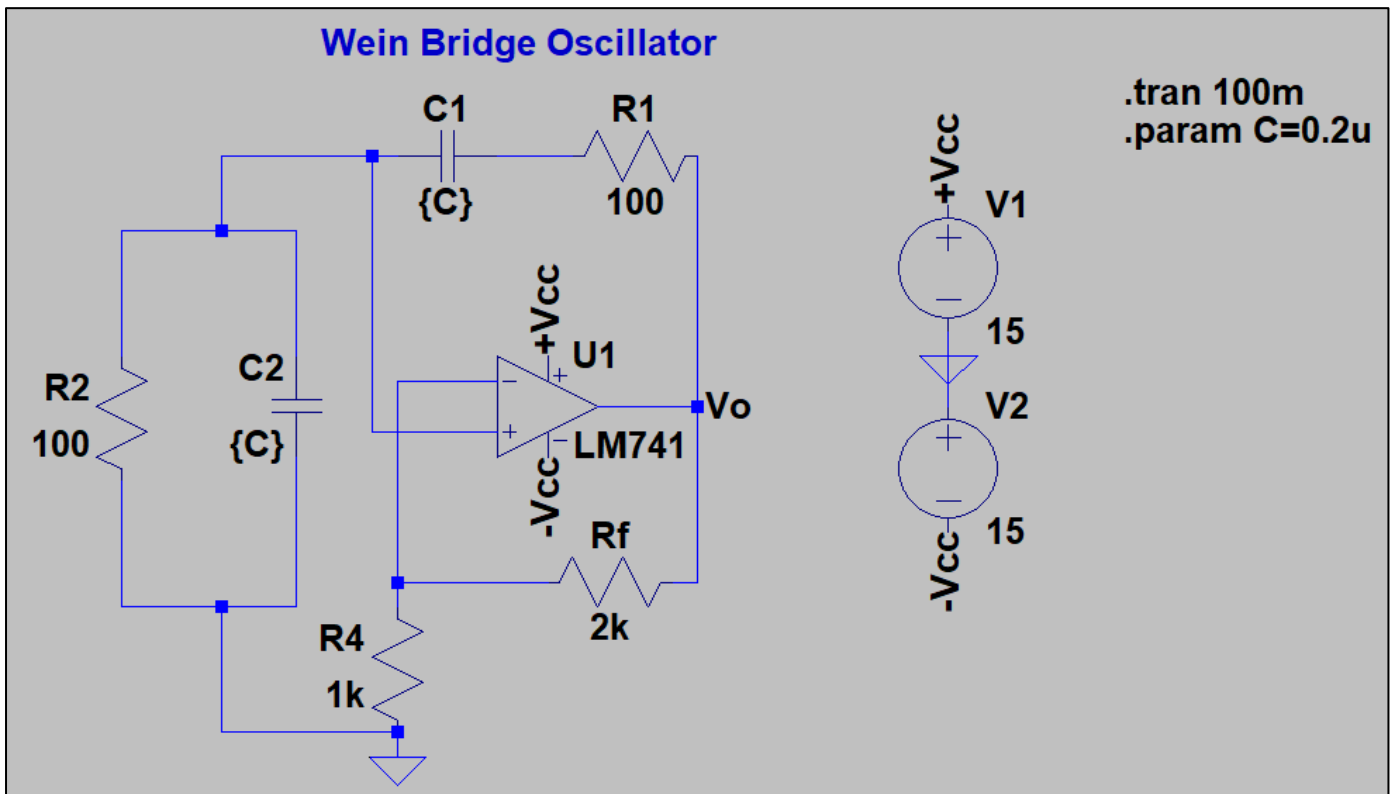

Results

Oscillator	Theoretical value of oscillator frequency	Best simulated value of oscillator frequency
RC phase shift oscillator C = 0.1uF	$\frac{1}{2\pi RC\sqrt{6}} = \frac{1}{2\pi \times 0.1\mu \times 100\sqrt{6}}$ = 6.497 kHz	6.060 kHz
RC phase shift oscillator C = 0.2uF	$\frac{1}{2\pi RC\sqrt{6}} = \frac{1}{2\pi \times 0.2\mu \times 100\sqrt{6}}$ = 3.249 kHz	3.085 kHz
Wein Bridge oscillator C= 0.1uF	$\frac{1}{2\pi RC} = \frac{1}{2\pi \times 0.1\mu \times 100}$ = 15.915 kHz	13.705 kHz
Wein Bridge oscillator C= 0.2uF	$\frac{1}{2\pi RC} = \frac{1}{2\pi \times 0.2\mu \times 100}$ = 7.958 kHz	7.437 kHz